

Electrical Science - I


(IEC-102)

Lecture-06

Capacitors and Inductors


The Capacitor

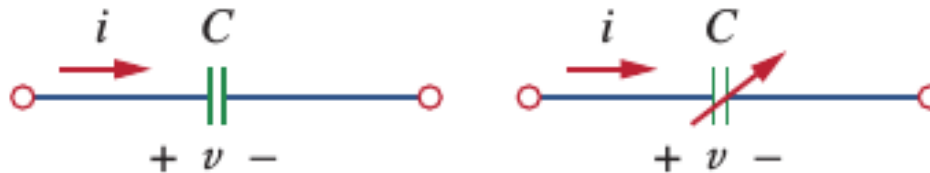- The ideal capacitor is a passive element with circuit symbol



The Capacitor

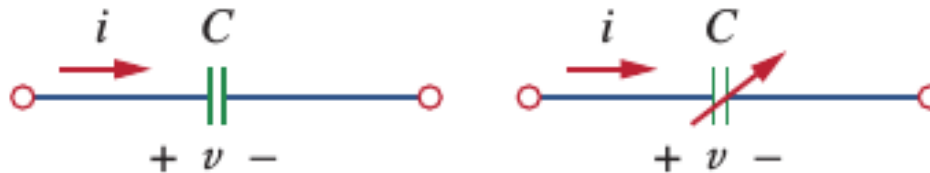- The ideal capacitor is a passive element with circuit symbol




- The current-voltage relation is

$$i = C \frac{dv}{dt}$$

The Capacitor

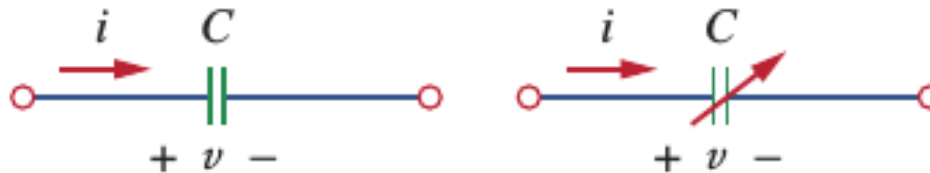- The ideal capacitor is a passive element with circuit symbol



- The current-voltage relation is

$$i = C \frac{dv}{dt}$$

- The capacitance C is measured in farads (F)

The Capacitor

- The voltage-current relation is

$$v(t) = \frac{1}{C} \int_{t_0}^t i(t) dt + v(t_0)$$

The Capacitor

- The voltage-current relation is

$$v(t) = \frac{1}{C} \int_{t_0}^t i(t) dt + v(t_0)$$

$$v(t) = \frac{1}{C} \int_{-\infty}^t i(t) dt$$

The Capacitor

- **The voltage-current relation is**

$$v(t) = \frac{1}{C} \int_{t_0}^t i(t) dt + v(t_0)$$

$$v(t) = \frac{1}{C} \int_{-\infty}^t i(t) dt$$

- **Instantaneous power**

$$p(t) = v(t)i(t) = Cv(t) \frac{dv(t)}{dt}$$

The Capacitor

□ Energy stored in a capacitor

$$w = \int_{-\infty}^t p dt = C \int_{-\infty}^t v \frac{dv}{dt} dt = C \int_{v(-\infty)}^{v(t)} v dv = \frac{1}{2} C v^2 \Big|_{v(-\infty)}^{v(t)}$$

The Capacitor

□ Energy stored in a capacitor

$$w = \int_{-\infty}^t p dt = C \int_{-\infty}^t v \frac{dv}{dt} dt = C \int_{v(-\infty)}^{v(t)} v dv = \frac{1}{2} C v^2 \Big|_{v(-\infty)}^{v(t)}$$


$$w = \frac{1}{2} C v^2$$

if

$$v(-\infty) = 0$$

Some Capacitors

Typical values range from pF to μF

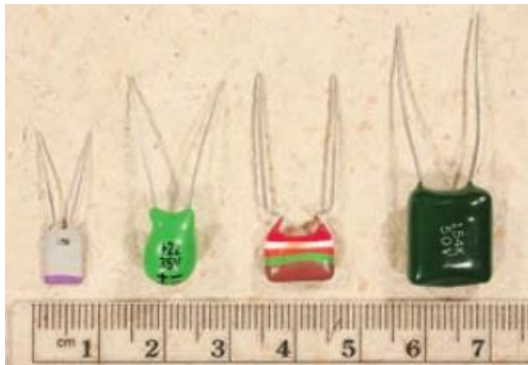

Key Capacitor Behaviors

- Acts as an open circuit to dc (in steady state).

Key Capacitor Behaviors


- ❑ Acts as an open circuit to dc (in steady state).
- ❑ Voltage across a capacitor cannot change abruptly.

Key Capacitor Behaviors

- ❑ Acts as an open circuit to dc (in steady state).
- ❑ Voltage across a capacitor cannot change abruptly.
- ❑ Ideal capacitors does not dissipate energy.


Key Capacitor Behaviors

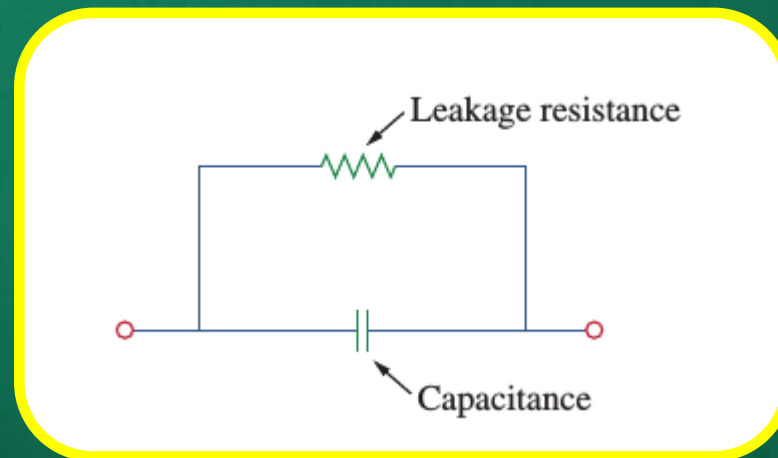- ❑ Acts as an open circuit to dc (in steady state).
- ❑ Voltage across a capacitor cannot change abruptly.
- ❑ Ideal capacitors does not dissipate energy.
- ❑ Non-ideal capacitor has a leakage resistance.




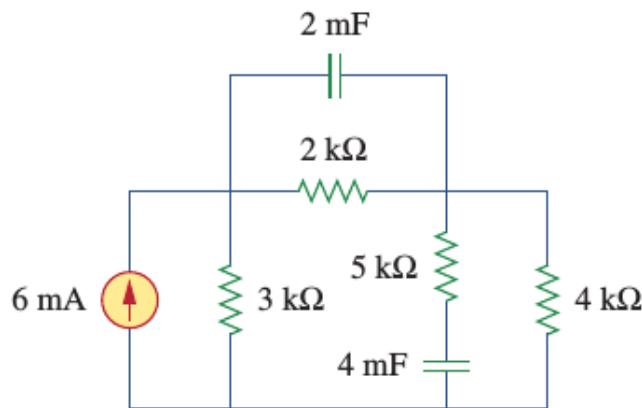
Example: Capacitor Energy

Calculate energy stored in each capacitor under DC conditions (or in steady state).



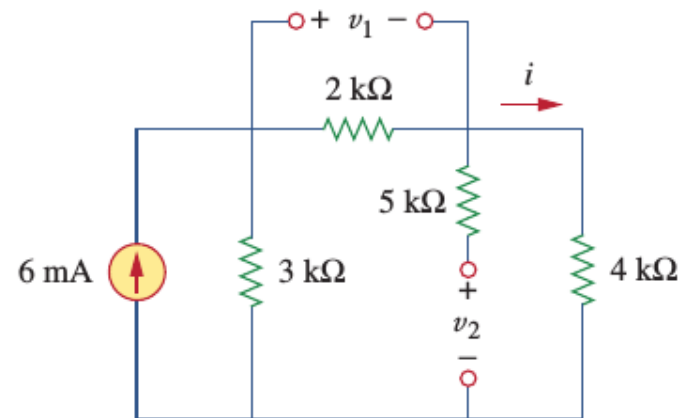
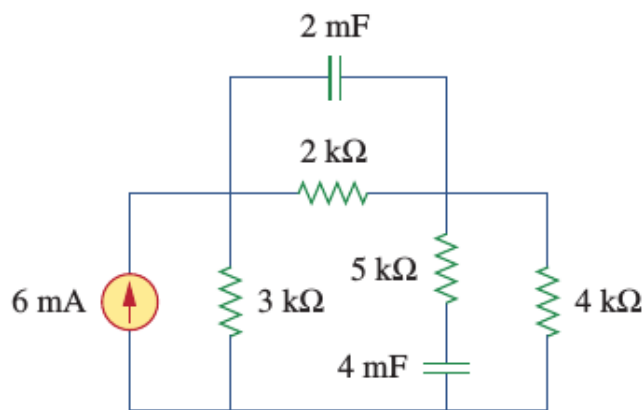
Example: Capacitor Energy

Calculate energy stored in each capacitor under DC conditions (or in steady state).



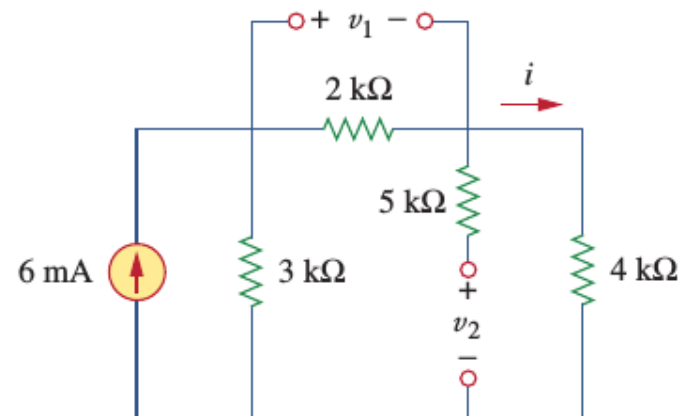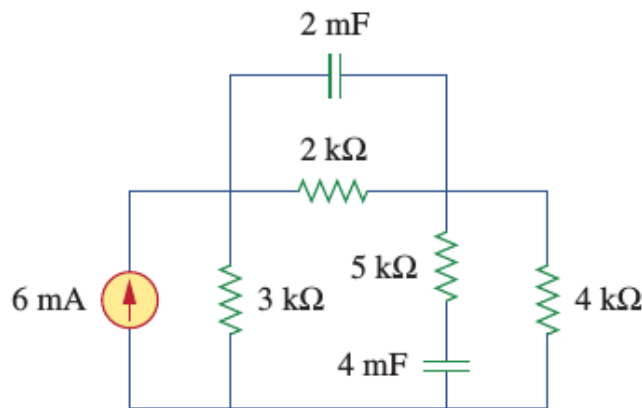Example: Capacitor Energy


Calculate energy stored in each capacitor under DC conditions (or in steady state).



Answer: $W_1 = 16 \text{ mJ}$; $W_2 = 128 \text{ mJ}$

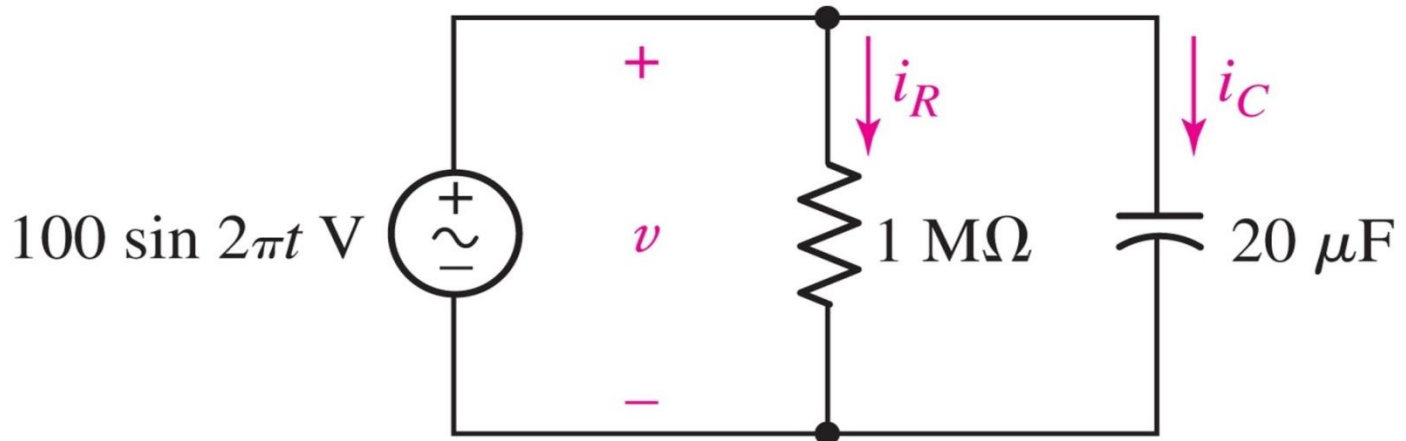
Example: Capacitor Energy

Determine the maximum energy stored in the capacitor, and plot i_R and i_C .



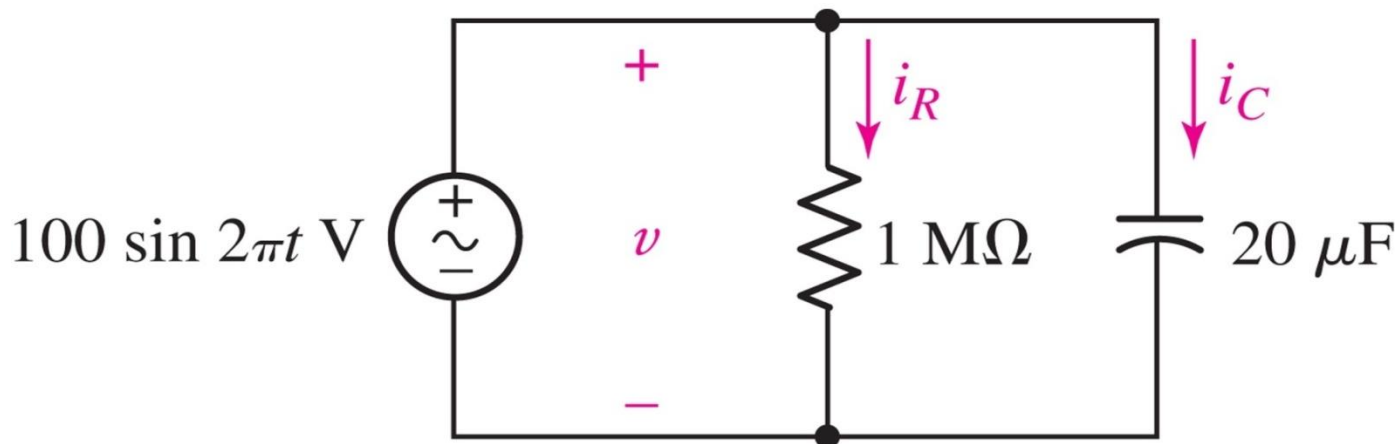Example: Capacitor Energy



Determine the maximum energy stored in the capacitor, and plot i_R and i_C .



Answer: Maximum energy = 0.1 J



The Inductor

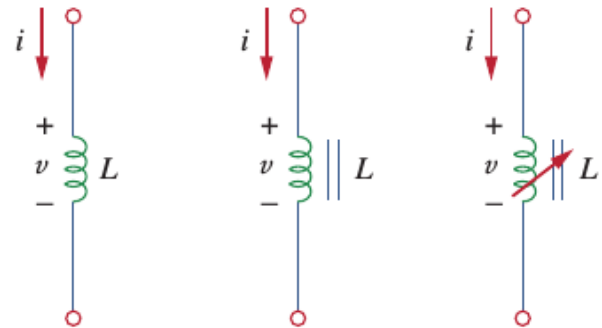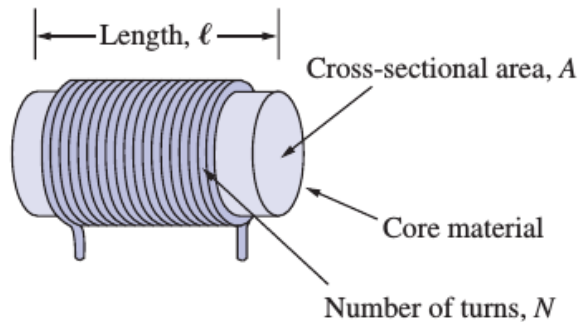- ❑ The ideal inductor is a passive element with circuit symbol



The Inductor

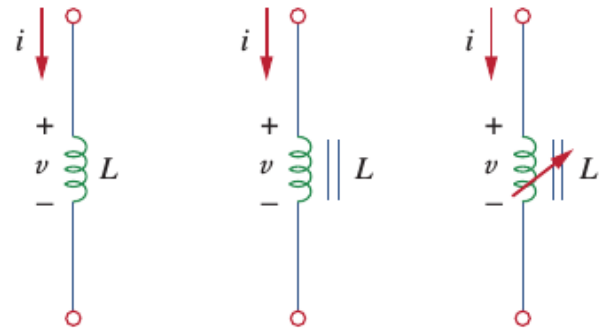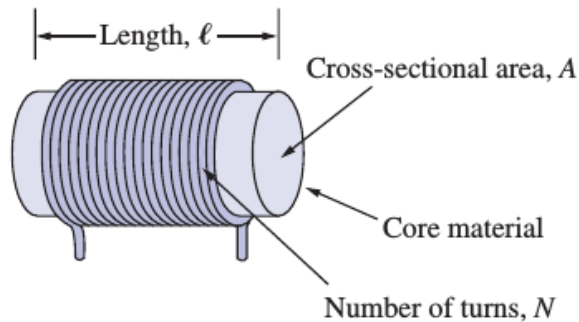- ❑ The ideal inductor is a passive element with circuit symbol





- ❑ The current-voltage relation is

$$v = L \frac{di}{dt}$$

The Inductor

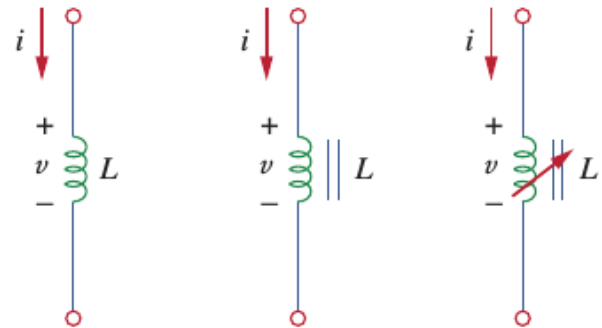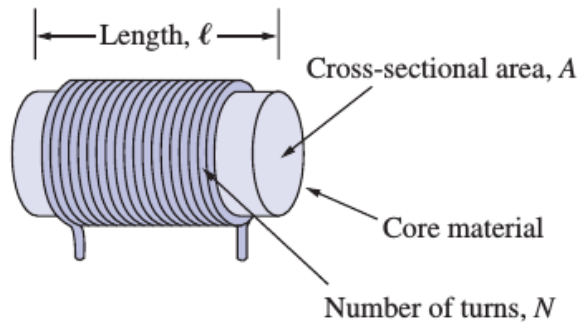- ❑ The ideal inductor is a passive element with circuit symbol



- ❑ The current-voltage relation is

$$v = L \frac{di}{dt}$$

- ❑ The inductance L is measured in Henry (H)

The Inductor

- The current-voltage is

$$i(t) = \frac{1}{L} \int_{-\infty}^t v(t) dt$$

The Inductor

- The current-voltage is

$$i(t) = \frac{1}{L} \int_{-\infty}^t v(t) dt$$

- Energy stored in an inductor


$$w = \frac{1}{2} Li^2$$

if

$$i(-\infty) = 0$$

Some Inductors

Typical values range from μH to H

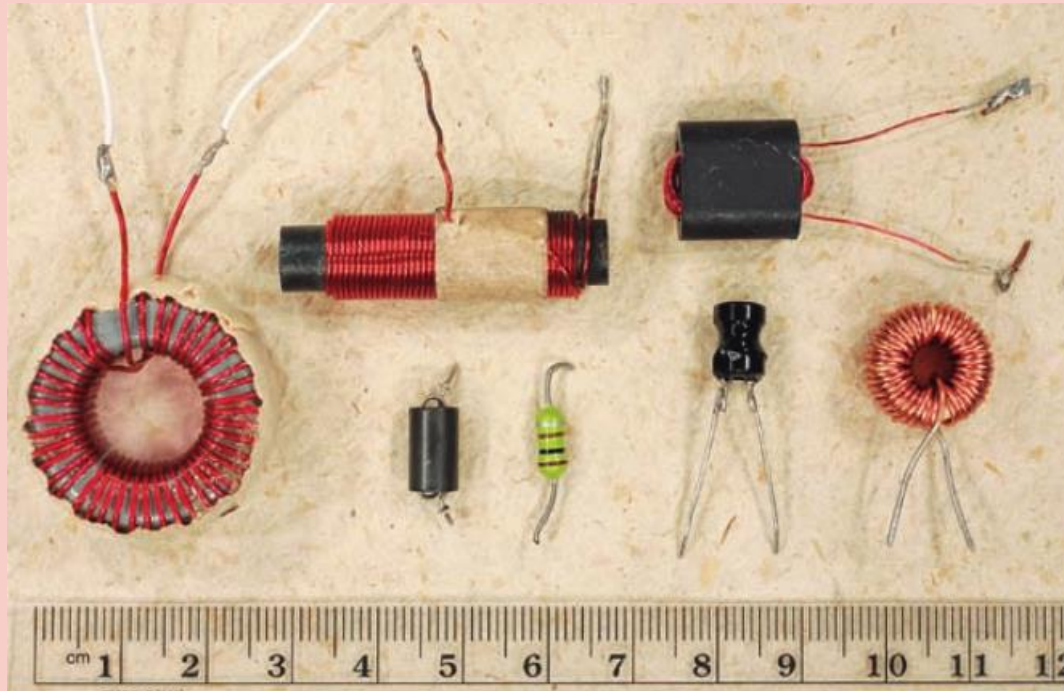

Key Inductor Behaviors

- Acts as an short circuit to dc (in steady state).

Key Inductor Behaviors


- ❑ Acts as an short circuit to dc (in steady state).
- ❑ Current through inductor cannot change abruptly.

Key Inductor Behaviors

- ❑ Acts as an short circuit to dc (in steady state).
- ❑ Current through inductor cannot change abruptly.
- ❑ Ideal inductors does not dissipate energy.


Key Inductor Behaviors

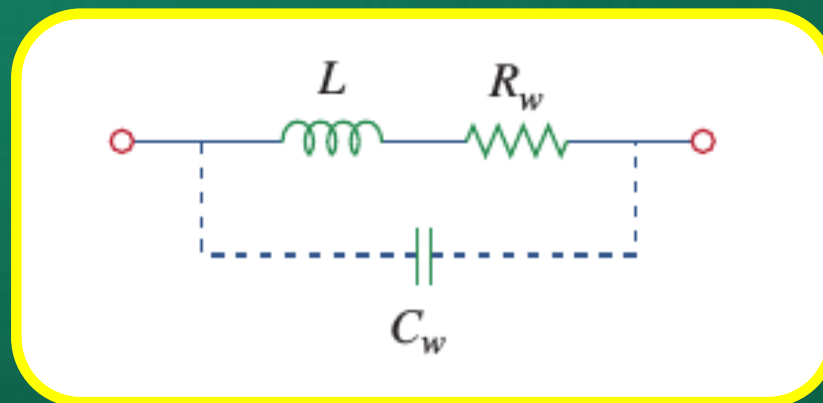- ❑ Acts as an short circuit to dc (in steady state).
- ❑ Current through inductor cannot change abruptly.
- ❑ Ideal inductors does not dissipate energy.
- ❑ Non-ideal inductor can be modeled as shown.



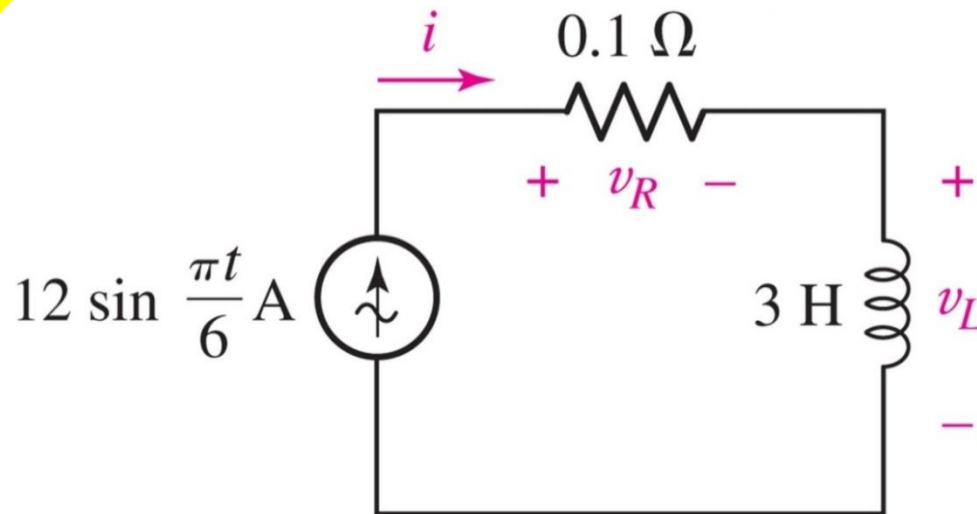
Example: Energy in L

Determine the maximum energy stored in the inductor, and find the energy lost by resistor from $t = 0$ to $t = 6$ s.



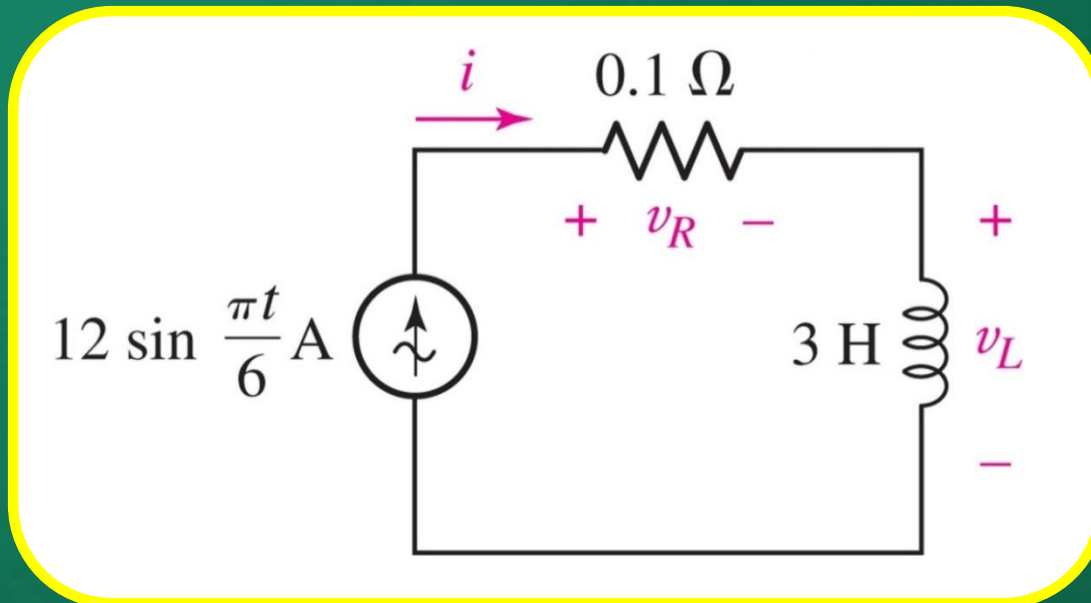Example: Energy in L


Determine the maximum energy stored in the inductor, and find the energy lost by resistor from $t = 0$ to $t = 6$ s.



Answer: 216 J, 43.2 J



Example: Simplifying LC Circuit

Simplify the circuit

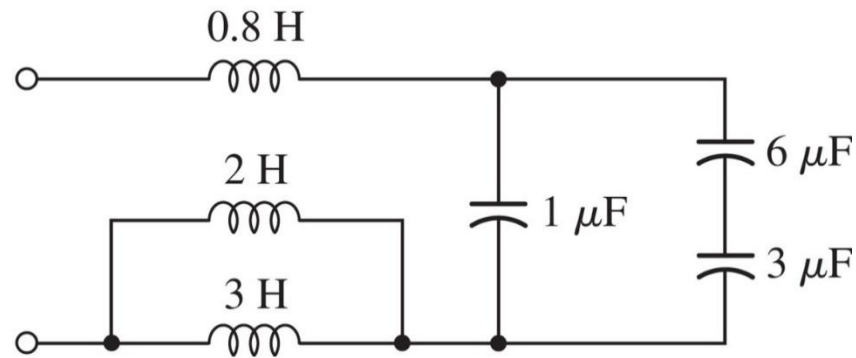


Example: Simplifying LC Circuit

Simplify the circuit

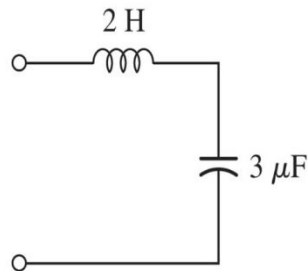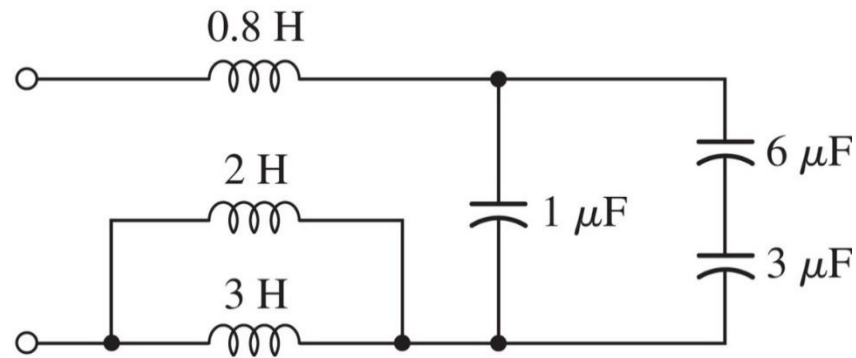

Nodal Equation for an RLC Circuit

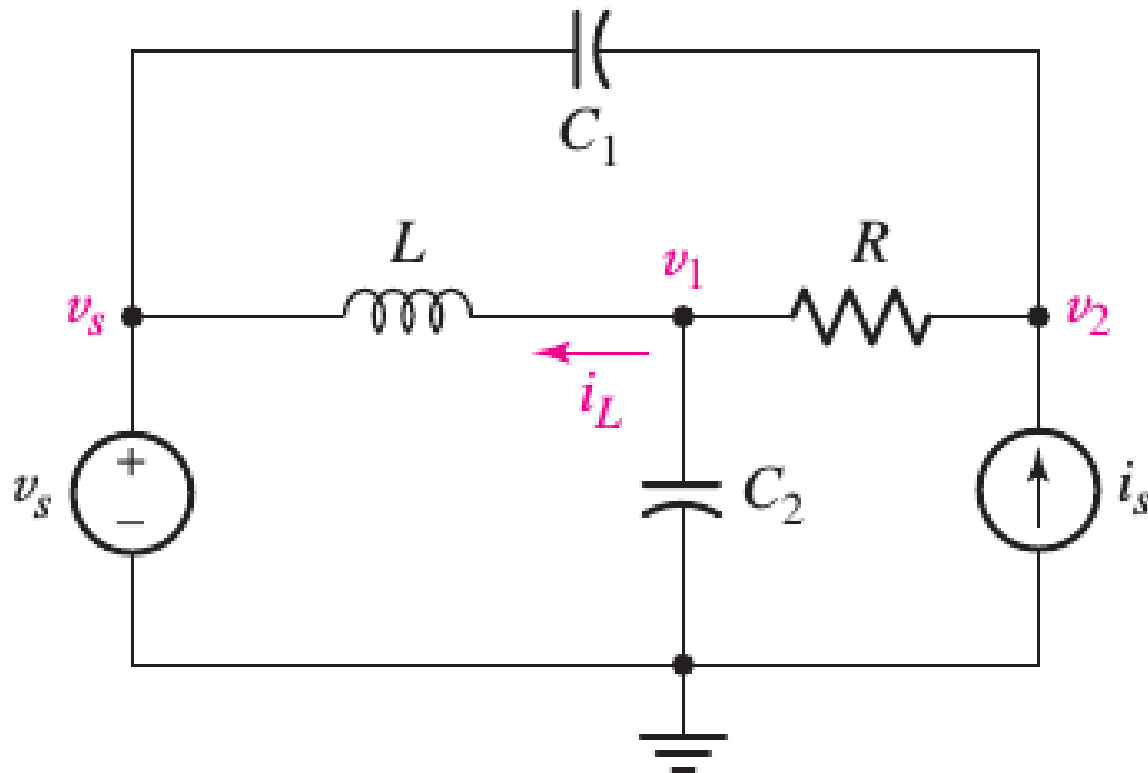

Nodal Equation for an RLC Circuit

$$\frac{1}{L} \int_{t_0}^t (v_1 - v_s) dt' + i_L(t_0) + \frac{v_1 - v_2}{R} + C_2 \frac{dv_1}{dt} = 0$$

Nodal Equation for an RLC Circuit

$$\frac{1}{L} \int_{t_0}^t (v_1 - v_s) dt' + i_L(t_0) + \frac{v_1 - v_2}{R} + C_2 \frac{dv_1}{dt} = 0$$

$$C_1 \frac{d(v_2 - v_s)}{dt} + \frac{v_2 - v_1}{R} - i_s = 0$$

Nodal Equation for an RLC Circuit

$$\frac{1}{L} \int_{t_0}^t (v_1 - v_s) dt' + i_L(t_0) + \frac{v_1 - v_2}{R} + C_2 \frac{dv_1}{dt} = 0$$


$$C_1 \frac{d(v_2 - v_s)}{dt} + \frac{v_2 - v_1}{R} - i_s = 0$$

$$\frac{v_1}{R} + C_2 \frac{dv_1}{dt} + \frac{1}{L} \int_{t_0}^t v_1 dt' - \frac{v_2}{R} = \frac{1}{L} \int_{t_0}^t v_s dt' - i_L(t_0)$$


$$-\frac{v_1}{R} + \frac{v_2}{R} + C_1 \frac{dv_2}{dt} = C_1 \frac{dv_s}{dt} + i_s$$

Source Free RL and RC Circuits

The Source-Free RL Circuit

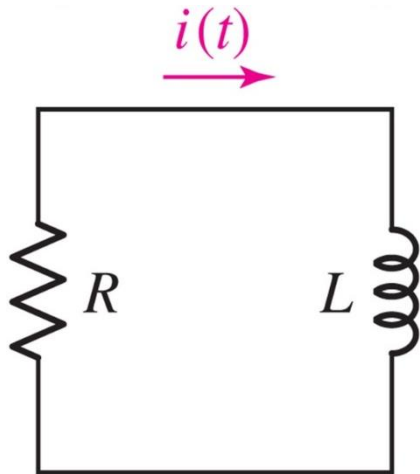


The Source-Free RL Circuit

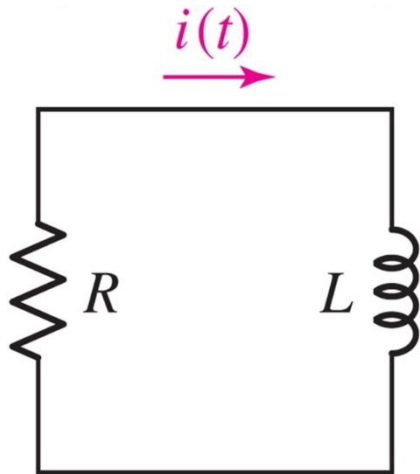

Applying KVL

$$\frac{di}{dt} + \frac{R}{L}i = 0$$

The Source-Free RL Circuit

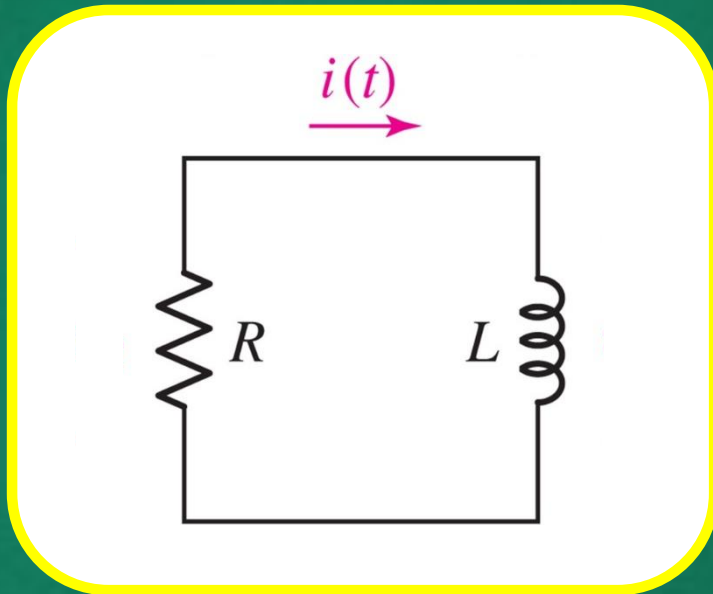


Applying KVL

$$\frac{di}{dt} + \frac{R}{L}i = 0$$

We can solve for the natural response if we know the initial condition $i(0)=I_0$

The Source-Free RL Circuit

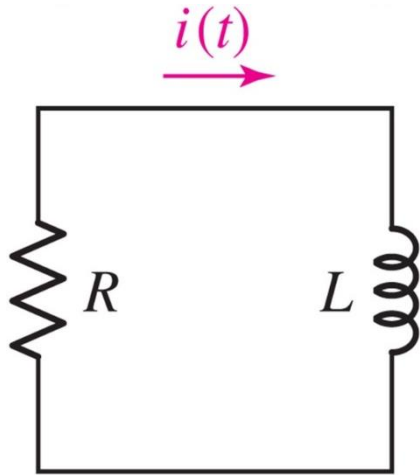


Applying KVL

$$\frac{di}{dt} + \frac{R}{L}i = 0$$

We can solve for the natural response if we know the initial condition $i(0)=I_0$

$$i(t) = I_0 e^{-Rt/L} \text{ for } t \geq 0$$

Example: RL with a Switch

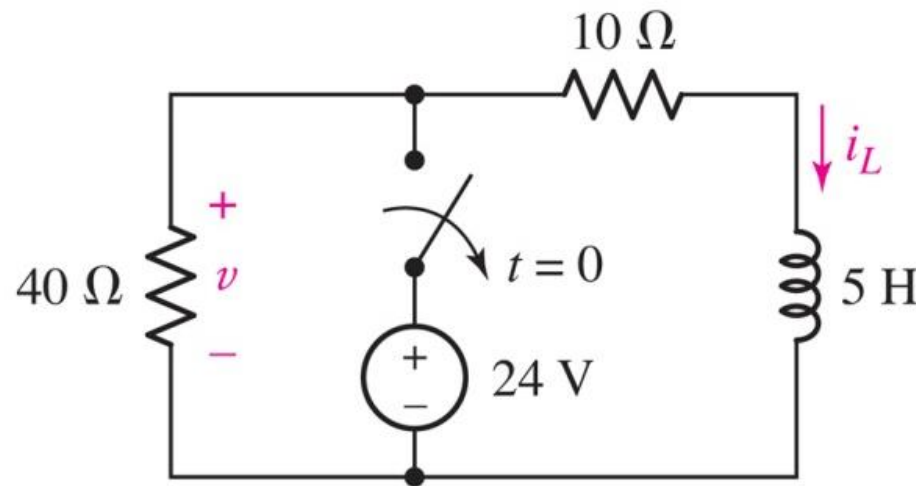

Show that the voltage $v(t)$ will be -12.99 V at $t = 200\text{ ms}$
(Assume that switch is in closed position since very long time before it is open)

The Exponential Response

$$i(t) = I_0 e^{-t/\tau} \text{ for } t \geq 0$$

$$\tau = L/R$$

The Exponential Response

$$i(t) = I_0 e^{-t/\tau} \text{ for } t \geq 0$$

$$\tau = L/R$$

The time constant τ determines the rate of decay.

The Exponential Response

$$i(t) = I_0 e^{-t/\tau} \text{ for } t \geq 0$$

$$\tau = L/R$$

The time constant τ determines the rate of decay.




The Exponential Response


$$i(t) = I_0 e^{-t/\tau} \text{ for } t \geq 0$$

$$\tau = L/R$$

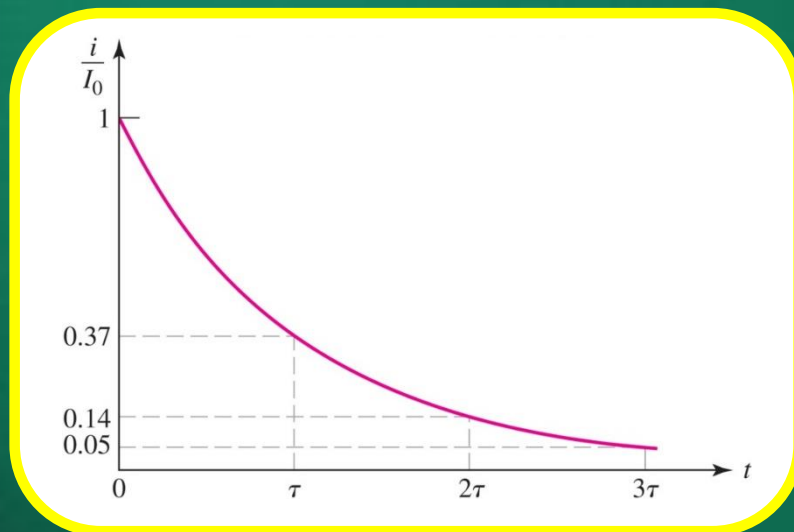
The time constant τ determines the rate of decay.



The Source-Free RC Circuit

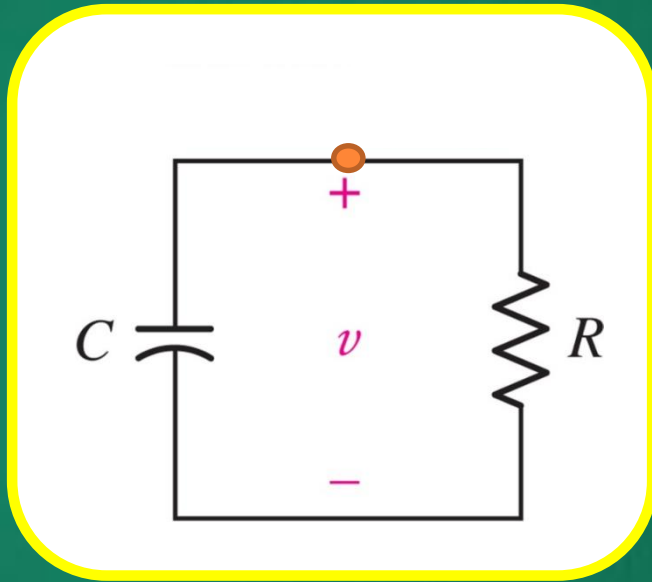


The Source-Free RC Circuit

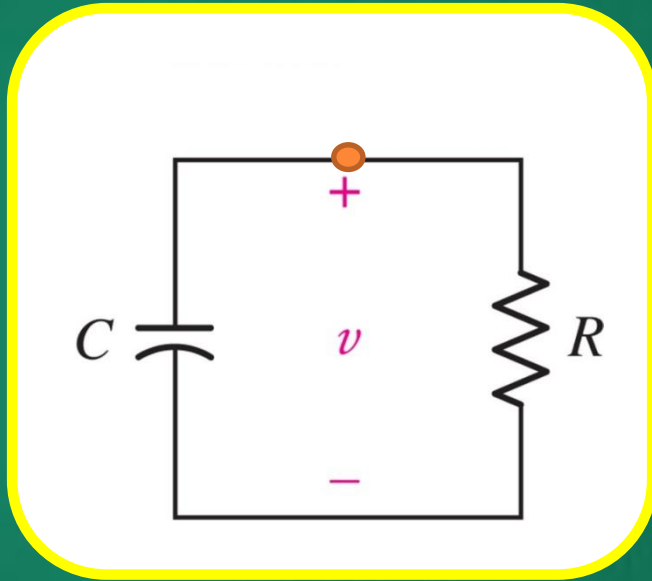

Applying KCL

$$\frac{dv}{dt} + \frac{1}{RC}v = 0$$

The Source-Free RC Circuit

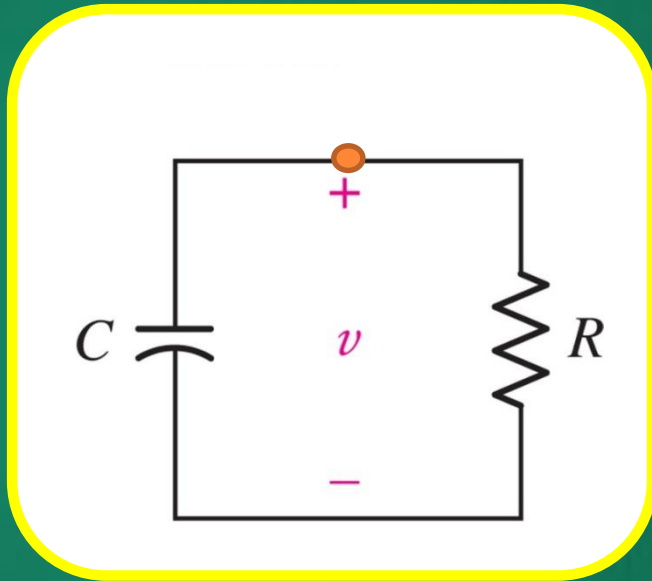


Applying KCL

$$\frac{dv}{dt} + \frac{1}{RC}v = 0$$

We can solve for the natural response if we know the initial condition $v(0)=V_0$

The Source-Free RC Circuit

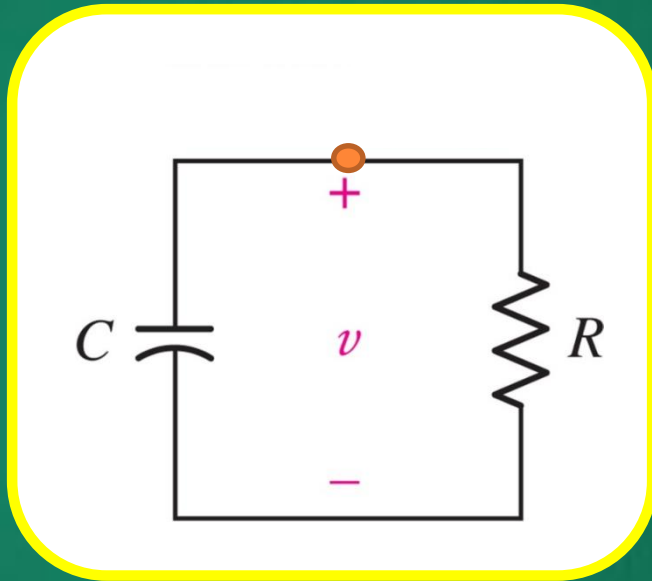


Applying KCL

$$\frac{dv}{dt} + \frac{1}{RC}v = 0$$


We can solve for the natural response if we know the initial condition $v(0)=V_0$

$$v(t) = V_0 e^{-t/RC} \text{ for } t \geq 0$$

RC Natural Response

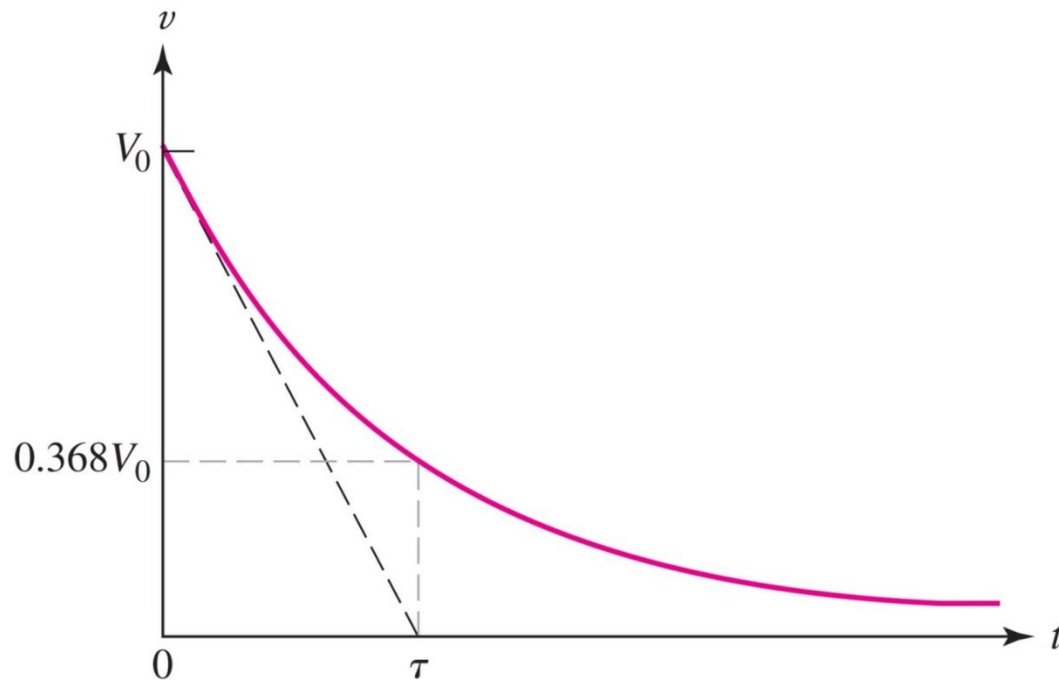


RC Natural Response

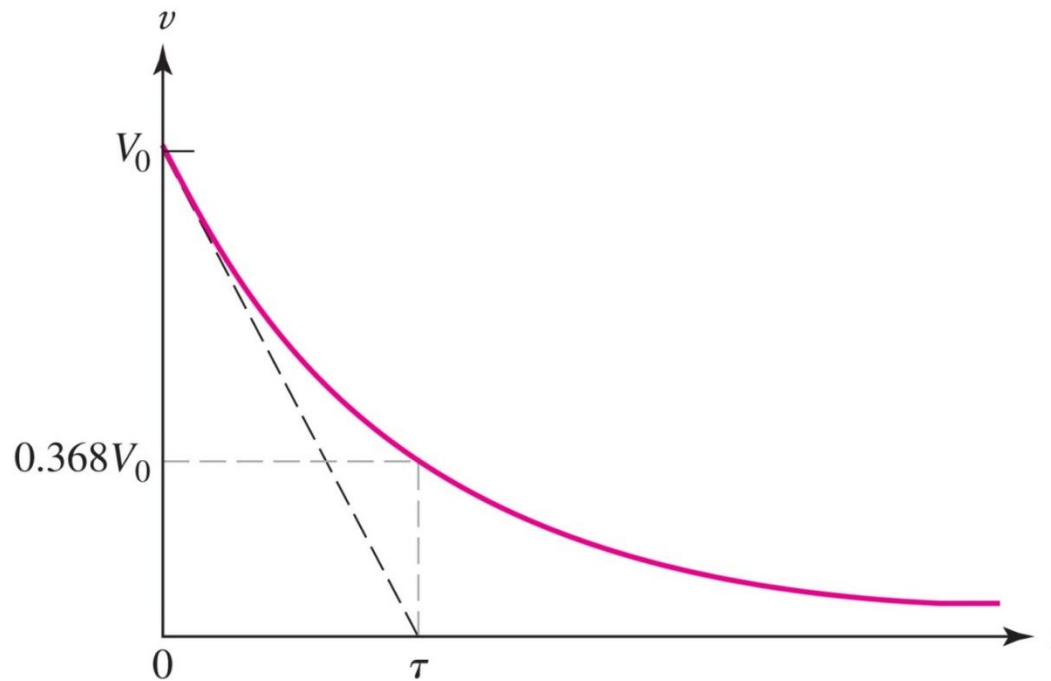

The time constant is $\tau = RC$

Example: Source Free RC Circuit

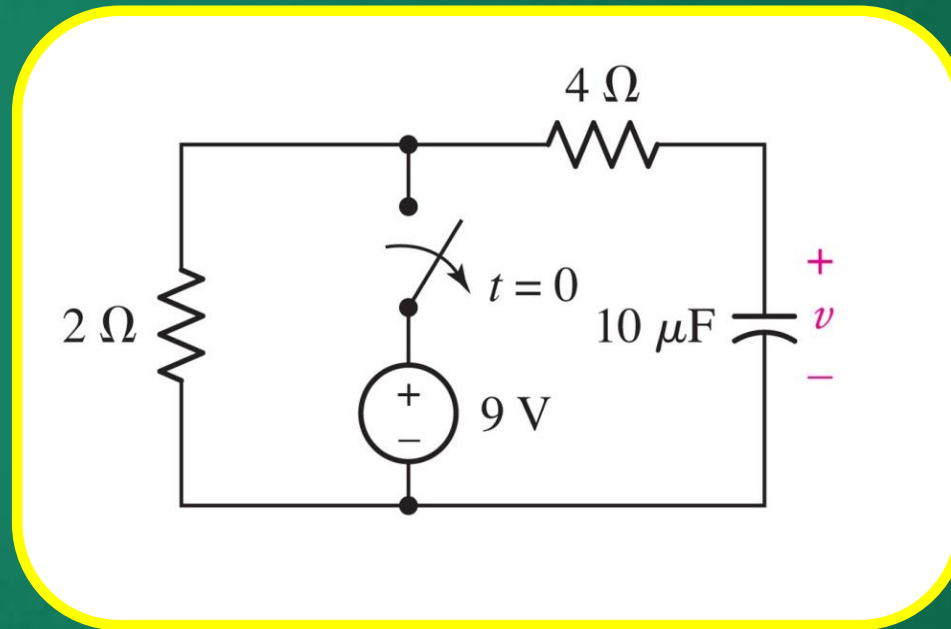

Show that the voltage $v(t)$ is 321 mV at $t = 200\ \mu\text{s}$.
(Assume that switch is in closed position since very long time before it is open)