

Solutions to Problem Sheet-4

IEC102

Q1. The Thevenin equivalent at terminals a-b of the linear network shown in Fig. Q1 is to be determined by measurement. When a $10\text{ k}\Omega$ resistor is connected to terminals a-b, the voltage V_{ab} is measured as 6 V . When a $30\text{ k}\Omega$ resistor is connected to the terminals, V_{ab} is measured as 12 V .

Determine

- The Thevenin equivalent at terminals a-b.
- V_{ab} when a $20\text{ k}\Omega$ resistor is connected to the terminals a-b.


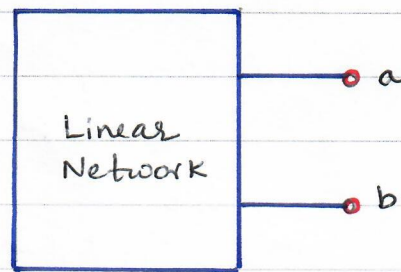


Fig. Q1

Sol.

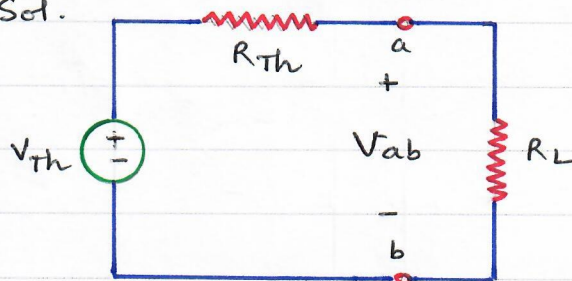

When $R_L = 10\text{ k}\Omega$; $V_{ab} = 6\text{ V}$

$R_L = 30\text{ k}\Omega$ $V_{ab} = 12\text{ V}$

$$V_{Th} \quad V_{ab} = \frac{V_{Th}}{R_{Th} + R_L} \times R_L$$

$$\Rightarrow V_{Th} R_L = V_{ab} (R_{Th} + R_L)$$

$$6 (R_{Th} + 10\text{ K}) = V_{Th} \times 10\text{ K} \quad \dots (1)$$

$$12 (R_{Th} + 30\text{ K}) = V_{Th} \times 30\text{ K} \quad \dots (2)$$

$$\frac{30}{10} = \frac{12}{6} \frac{(R_{Th} + 30K)}{(R_{Th} + 10K)}$$

$$\Rightarrow 3 = \frac{2(R_{Th} + 30K)}{(R_{Th} + 10K)}$$


$$\Rightarrow 3(R_{Th} + 10K) = 2(R_{Th} + 30K)$$

$$R_{Th} = 60K - 30K = 30K \Omega$$

$$V_{Th} \times 10K = 6(R_{Th} + 10K) = 6(30K + 10K)$$

$$V_{Th} \times 10K = 6 \times 40K$$

$$\Rightarrow V_{Th} = 24V$$

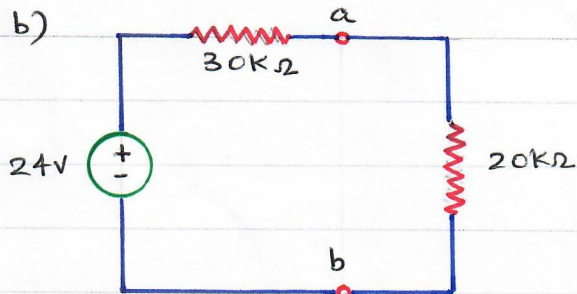

$$V_{ab} = 24 \times \frac{20K}{30K + 20K}$$

$$= 9.6V$$

Q2 For the bridge network shown in Fig. Q2, find R_{ab} and i .



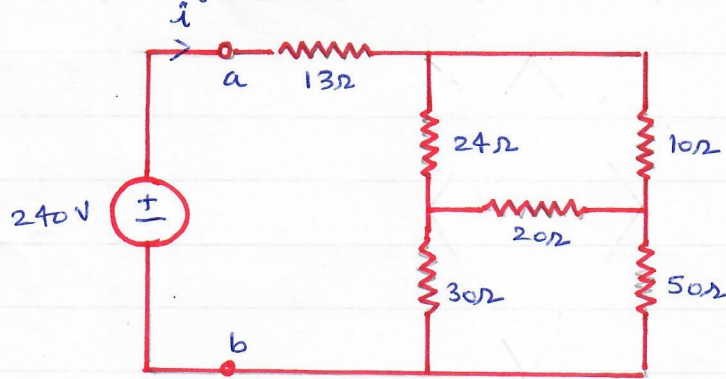
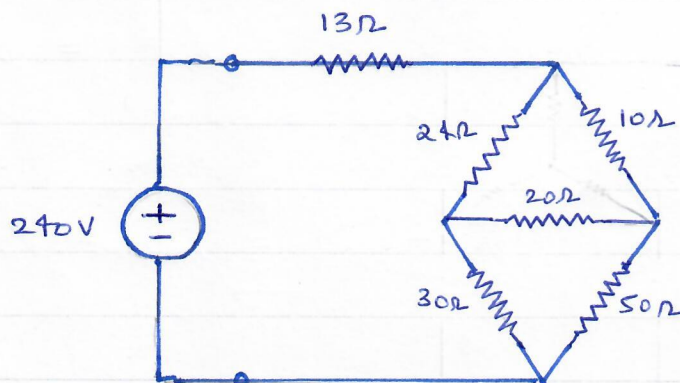


Fig. Q2



Sol. circuit can be redrawn as

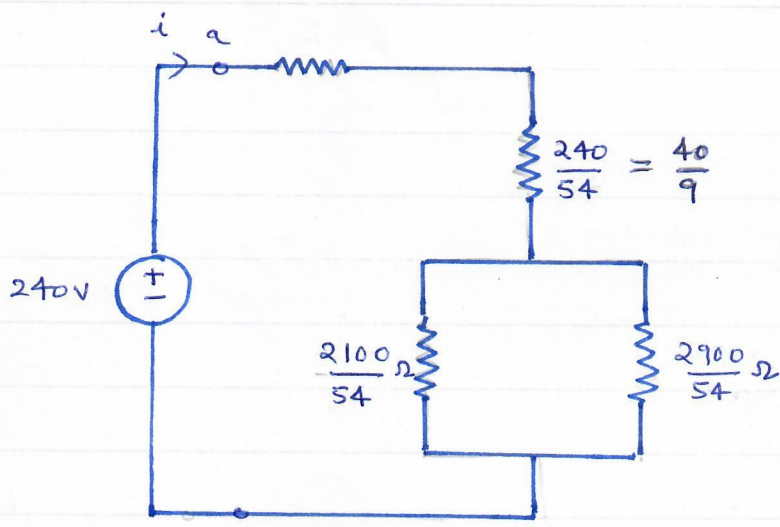

Transforming upper delta network to Y.

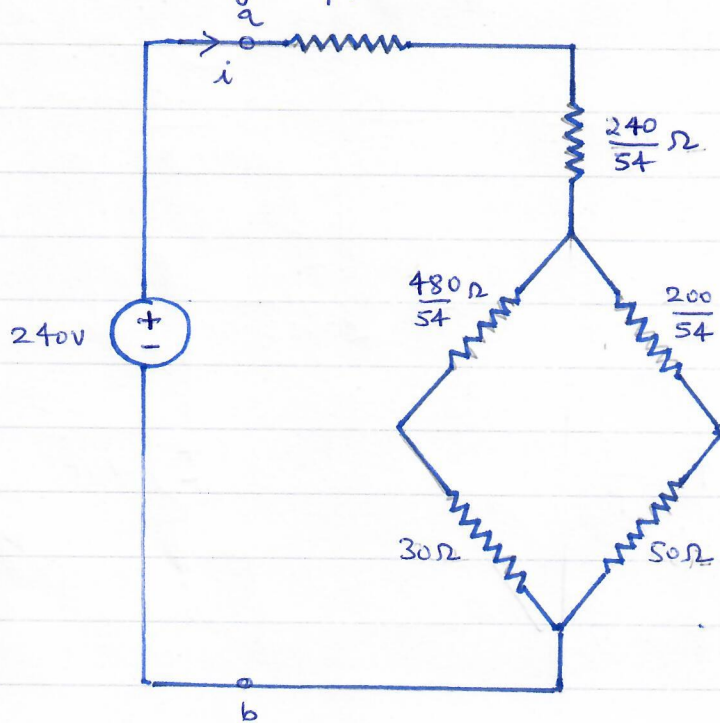



\Rightarrow

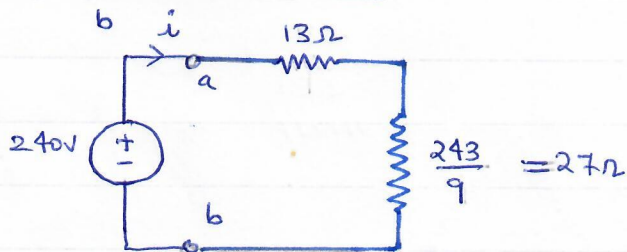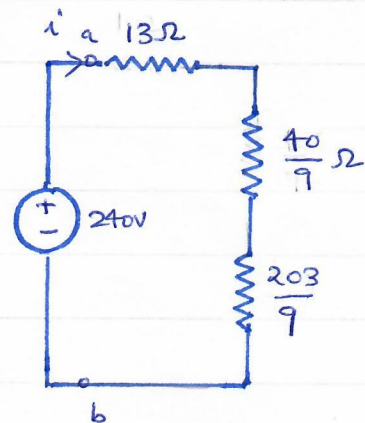

$$R_{ab} = 13 + 27 = 40\Omega$$

$$i' = \frac{240}{40} = 6A$$

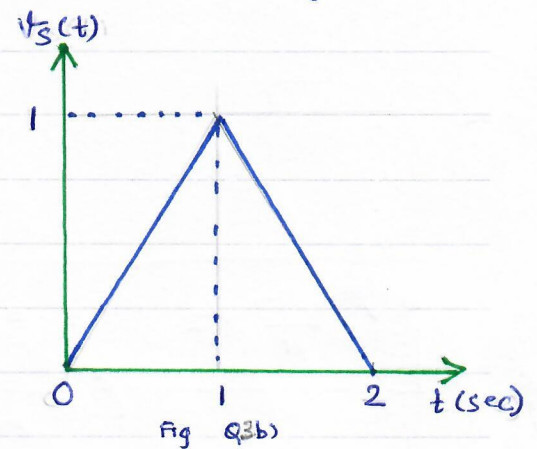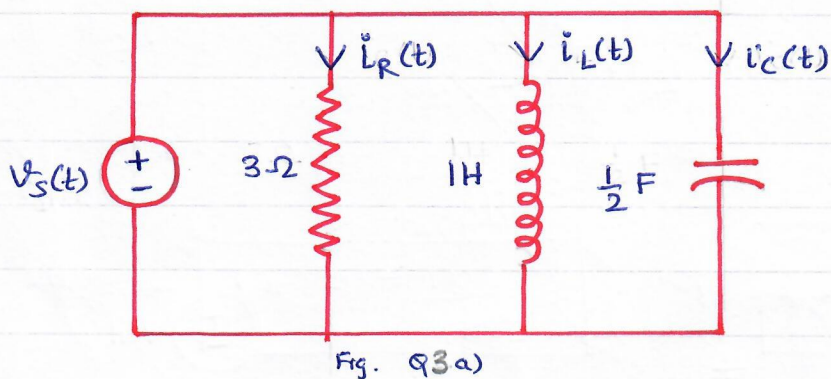- Q3) The voltage source $V_S(t)$ in the circuit shown in Fig. Q3a) has the source waveform as shown in Fig. Q3b)




- Sketch $i_R(t)$
- Sketch $i_C(t)$
- Sketch $i_L(t)$, assume $i_L(0) = 0$.

Sol. $i_R(t) = \frac{V_S(t)}{3}$; $i_C(t) = C \frac{dV_S(t)}{dt}$; $i_L(t) = \frac{1}{L} \int_0^t V_S(t) dt$

The voltage across all the elements is $V_S(t)$, as they are connected in parallel.

$$V_S(t) = \begin{cases} t & 0 \leq t < 1 \\ -t+2 & 1 \leq t \leq 2 \\ 0 & t > 2 \end{cases}$$

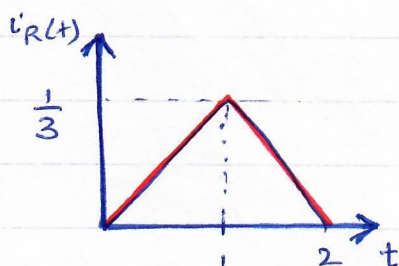
$$a) \quad i_R(t) = \frac{V_S(t)}{3} = \begin{cases} \frac{t}{3} & 0 \leq t < 1 \\ -\frac{t+2}{3} & 1 \leq t \leq 2 \\ 0 & t > 2 \end{cases}$$



$$b) \quad v_C(t) = C \frac{dv_S(t)}{dt} = \frac{1}{2} \frac{dv_S(t)}{dt} \quad \therefore C = \frac{1}{2} F$$

$$v_C = \begin{cases} \frac{1}{2} \frac{d}{dt}(t) & 0 \leq t < 1 \\ \frac{1}{2} \frac{d}{dt}(-t+2) & 1 \leq t \leq 2 \\ 0 & t > 2 \end{cases}$$

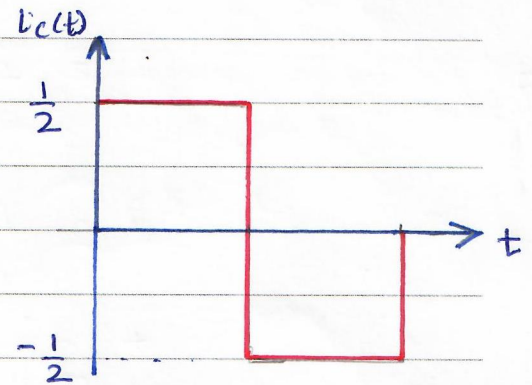
$$= \begin{cases} \frac{1}{2} & 0 \leq t < 1 \\ -\frac{1}{2} & 1 \leq t \leq 2 \\ 0 & t > 2 \end{cases}$$



$$c) \quad v_L(t) = \frac{1}{L} \int_{-\infty}^t v_S(t) dt = \frac{1}{L} \int_0^t v_S(t) dt = \int_0^t v_S(t) dt \quad \therefore L = 1 H$$

$$v_L(t) = \begin{cases} \int_0^t v_S(t) dt + v_L(0) & 0 \leq t < 1 \\ \int_1^t (-t+2) dt + v_L(1) & 1 \leq t \leq 2 \\ 0 + v_L(2) & t > 2 \end{cases}$$
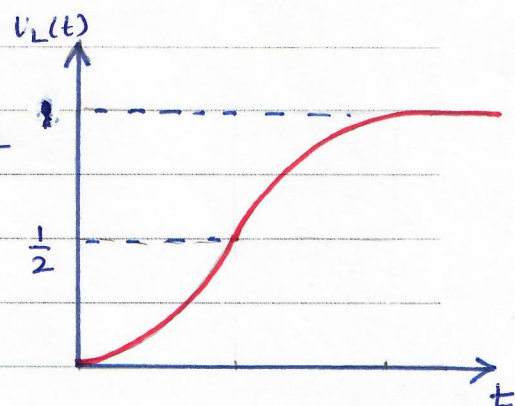
$$= \begin{cases} \frac{t^2}{2} & 0 \leq t < 1 \\ -\frac{t^2}{2} + 2t - 1 & 1 \leq t \leq 2 \\ 1 & t > 2 \end{cases}$$



Q4 For the circuit shown in Fig. Q4, calculate the value of 'R' that will make energy stored in the capacitor the same as that stored in the inductor under dc conditions.


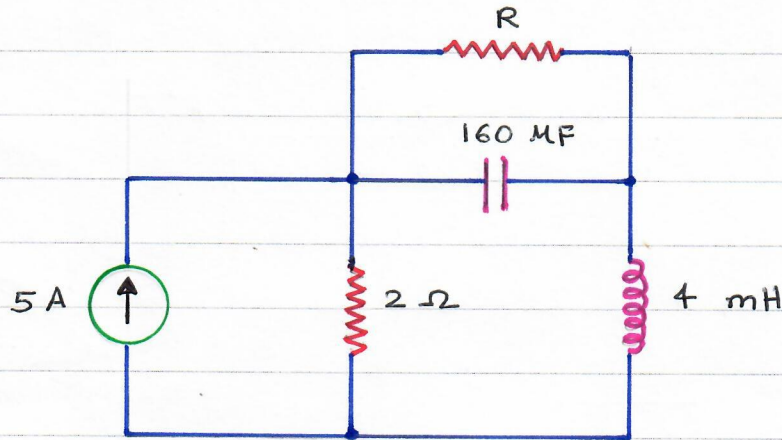


Fig. Q4

Sol. Under dc conditions capacitor acts as open circuit and inductor acts as short circuit.

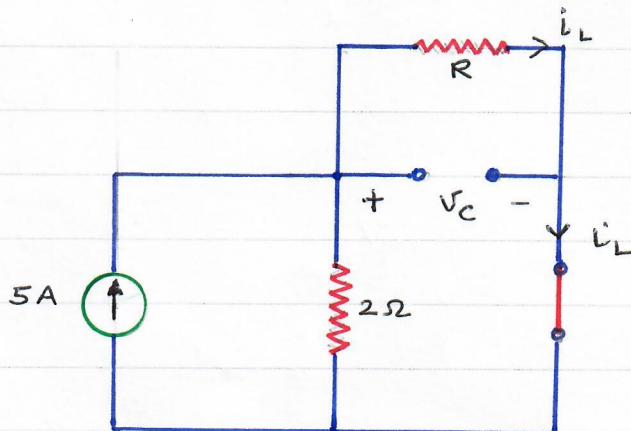The equivalent circuit under dc conditions is



$$i_L = 5 \times \frac{2}{2+R} = \frac{10}{R+2}$$

$$V_C = i_L R$$

$$= \frac{10R}{R+2}$$

$$\text{Energy stored in capacitor} = \frac{1}{2} C V_C^2 = W_C$$

$$\Rightarrow W_C = \frac{1}{2} \times 160 \times 10^{-6} \times \left(\frac{10R}{(R+2)} \right)^2$$

$$= \frac{1}{2} \times 160 \times 10^{-6} \times \frac{100R^2}{(R+2)^2}$$

$$= \frac{80 \times 10^{-4} R^2}{(R+2)^2}$$

$$\text{Energy stored in the inductor} = \frac{1}{2} L i_L^2 = W_L$$

$$= \frac{1}{2} \times 4 \times 10^{-3} \times \left(\frac{10}{R+2} \right)^2$$

$$= \frac{0.2}{(R+2)^2}$$

$$\text{If } W_C = W_L$$

$$\therefore \frac{80 \times 10^{-4} R^2}{(R+2)^2} = \frac{0.2}{(R+2)^2}$$

$$R^2 = \frac{0.2}{80 \times 10^{-4}} = 25$$

$$\therefore R = 5 \Omega$$