

Electrical Science - I

(IEC-102)

Lecture-03

Nodal & Mesh Analysis

Nodal and Mesh Analysis

- As circuits get more complicated, we need an organized method of applying **KVL**, **KCL**, and **Ohm's law**.

Nodal and Mesh Analysis



- ❑ As circuits get more complicated, we need an organized method of applying **KVL**, **KCL**, and **Ohm's law**.
- ❑ **Nodal analysis** assigns voltages to each node, and then we apply **KCL**.

Nodal and Mesh Analysis

- ❑ As circuits get more complicated, we need an organized method of applying **KVL**, **KCL**, and **Ohm's law**.
- ❑ **Nodal analysis** assigns voltages to each node, and then we apply **KCL**.
- ❑ **Mesh analysis** assigns currents to each mesh, and then we apply **KVL**.

The Nodal Analysis Method

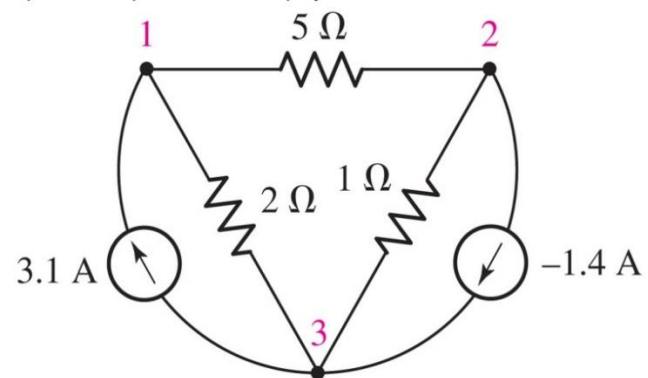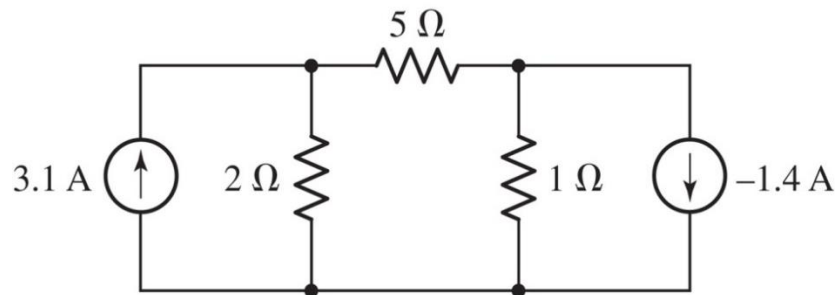- ❑ Identify the **nodes** in the given circuit.
- ❑ Choose one node among them as a **reference**.
- ❑ Assign voltages to every other node relative to a reference node.




In the circuit above, there are three nodes.

Choosing the Reference Node


- ❑ The bottom node, or
- ❑ the ground connection, if there is one, or
- ❑ a node with many connections

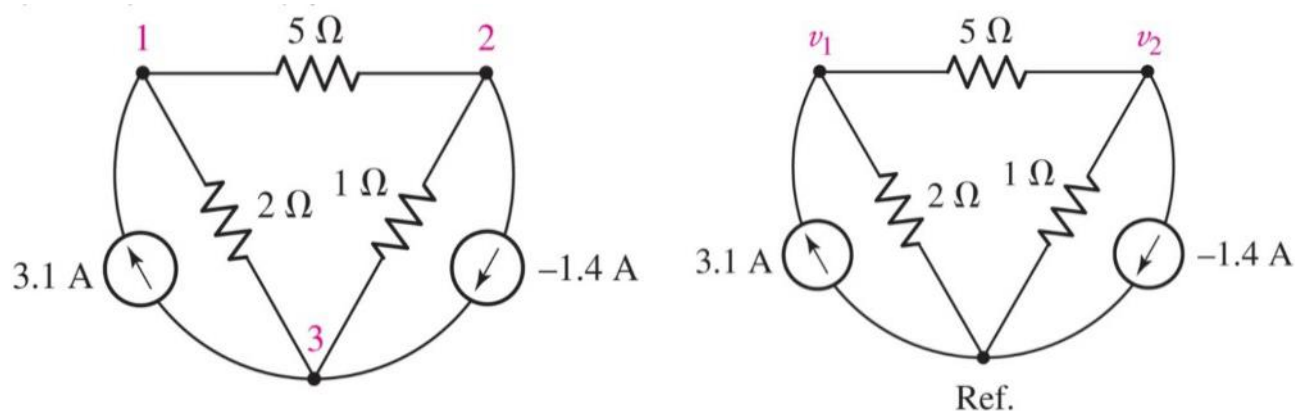Assign voltages to other nodes relative to reference.



Apply KCL to Find Voltages

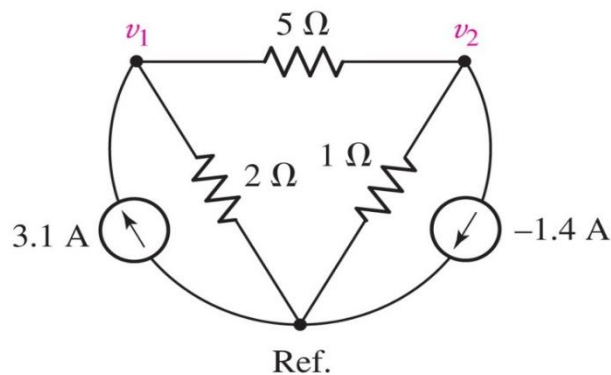
Apply **KCL** to **node 1** ($\Sigma_{\text{out}} = 0$) and **Ohm's law** to each resistor.



Apply KCL to Find Voltages

Apply **KCL** to **node 1** ($\Sigma_{\text{out}} = 0$) and **Ohm's law** to each resistor.

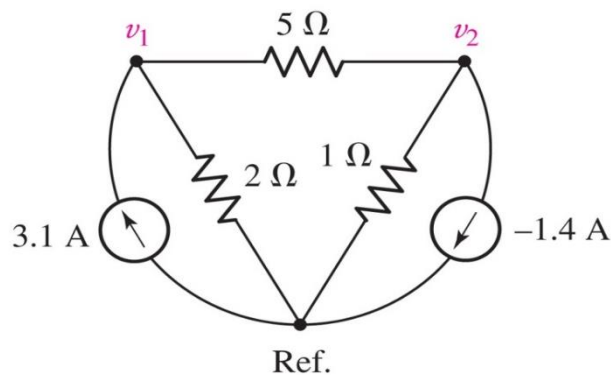
$$-3.1 + \frac{v_1}{2} + \frac{v_1 - v_2}{5} = 0$$



Apply KCL to Find Voltages

Apply **KCL** to **node 1** ($\Sigma_{\text{out}} = 0$) and **Ohm's law** to each resistor.

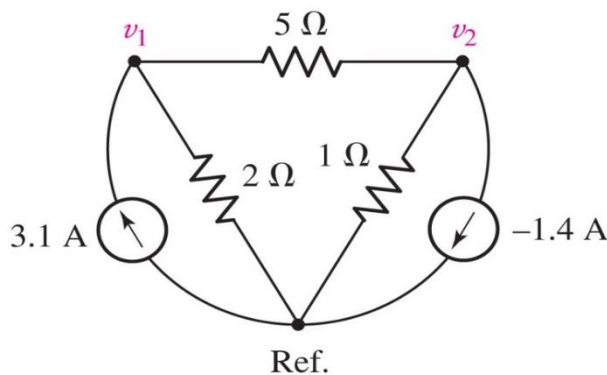
$$-3.1 + \frac{v_1}{2} + \frac{v_1 - v_2}{5} = 0$$



Note: the current flowing out of node 1 through the 5 Ω resistor is $(v_1 - v_2)/5$

Apply KCL to Find Voltages

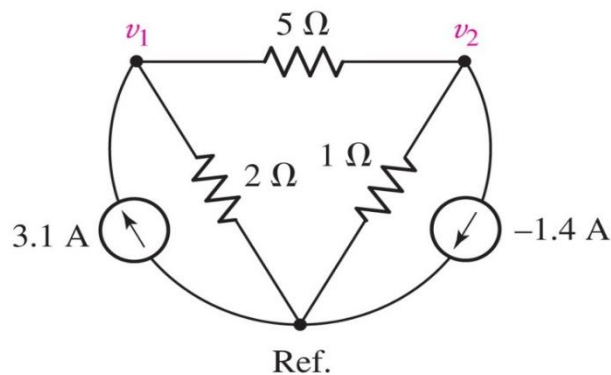
Apply **KCL** to **node 2** ($\Sigma_{\text{out}} = 0$) and Ohm's law to each resistor.



Apply KCL to Find Voltages

Apply **KCL** to **node 2** ($\Sigma_{\text{out}} = 0$) and Ohm's law to each resistor.

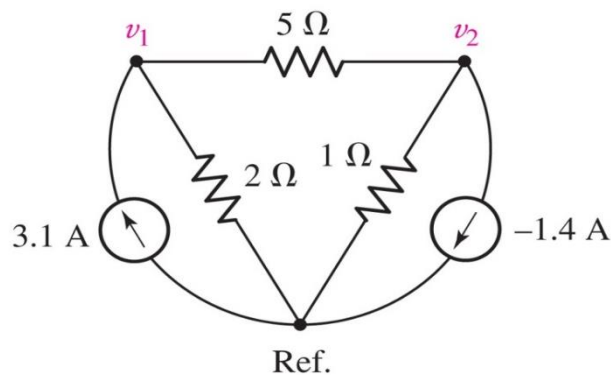
$$\frac{v_2}{1} + \frac{v_2 - v_1}{5} - 1.4 = 0$$



Apply KCL to Find Voltages

Apply **KCL** to **node 2** ($\Sigma_{\text{out}} = 0$) and Ohm's law to each resistor.
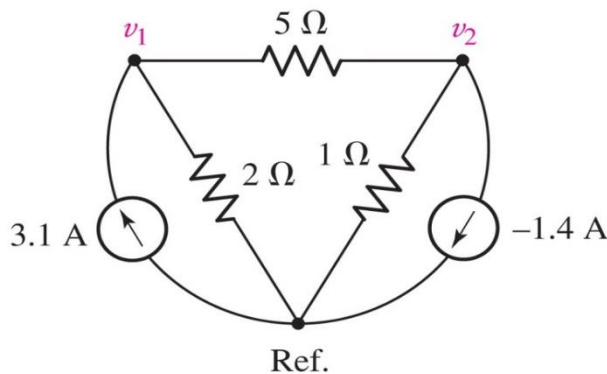
$$\frac{v_2}{1} + \frac{v_2 - v_1}{5} - 1.4 = 0$$




Note: the current flowing out of node 2 through the 5Ω resistor is $(v_2 - v_1)/5$

Solve for Node Voltages

$$-3.1 + \frac{v_1}{2} + \frac{v_1 - v_2}{5} = 0$$

$$\frac{v_2}{1} + \frac{v_2 - v_1}{5} - 1.4 = 0$$

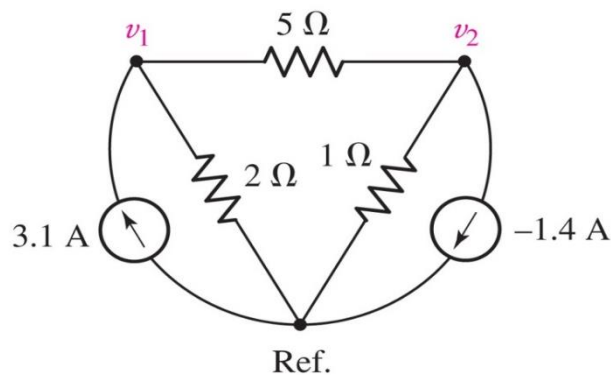We now have two equations for the two unknowns v_1 and v_2 and can be solved.




Solve for Node Voltages

$$-3.1 + \frac{v_1}{2} + \frac{v_1 - v_2}{5} = 0$$

$$\frac{v_2}{1} + \frac{v_2 - v_1}{5} - 1.4 = 0$$

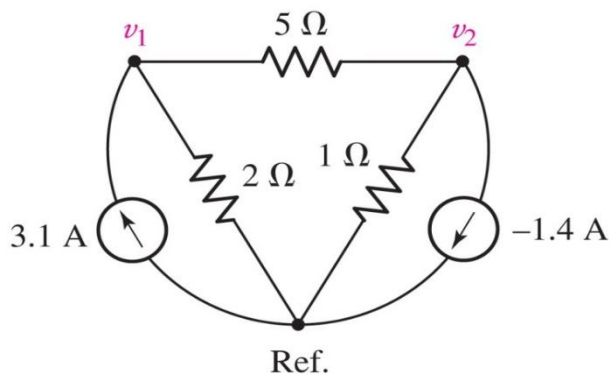
We now have two equations for the two unknowns v_1 and v_2 and can be solved.



$$v_1 = 5\text{ V and } v_2 = 2\text{ V}$$


Example: Nodal Analysis

Find the current i in the circuit.

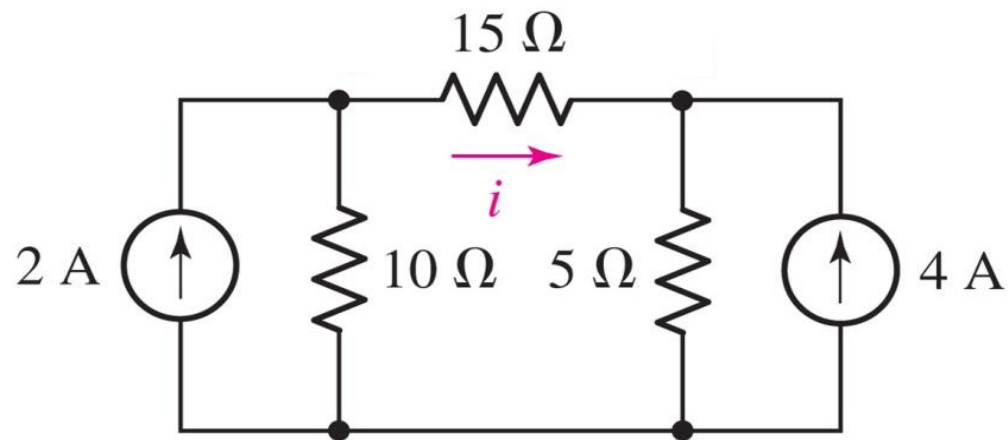


Example: Nodal Analysis

Find the current i in the circuit.

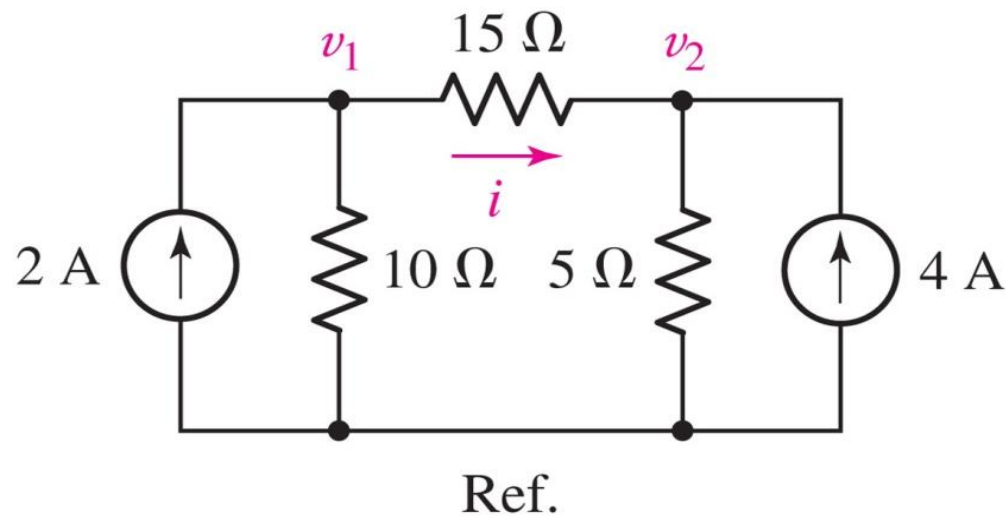

Example: Nodal Analysis


Find the current i in the circuit.

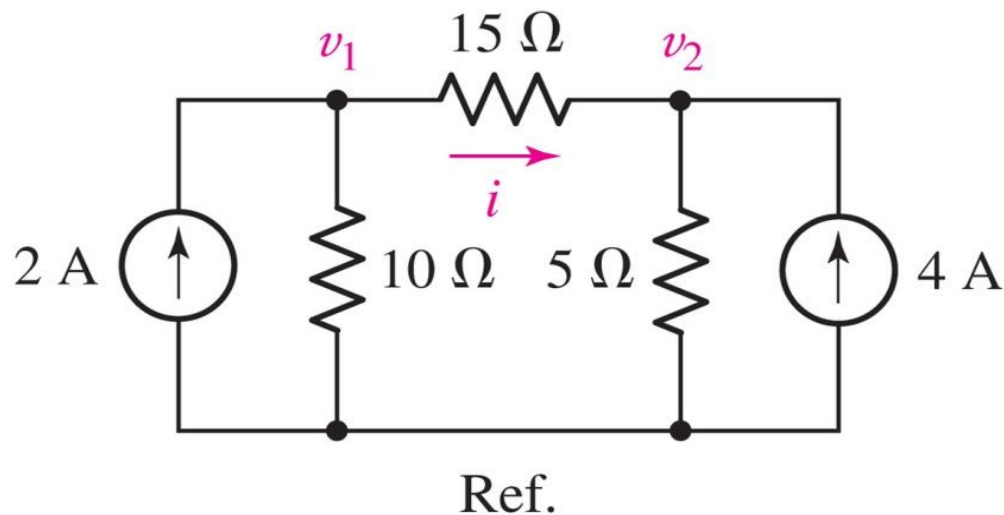

Answer: $i = 0$ (since $v_1 = v_2 = 20$ V)


Nodal Analysis: Dependent Source Example

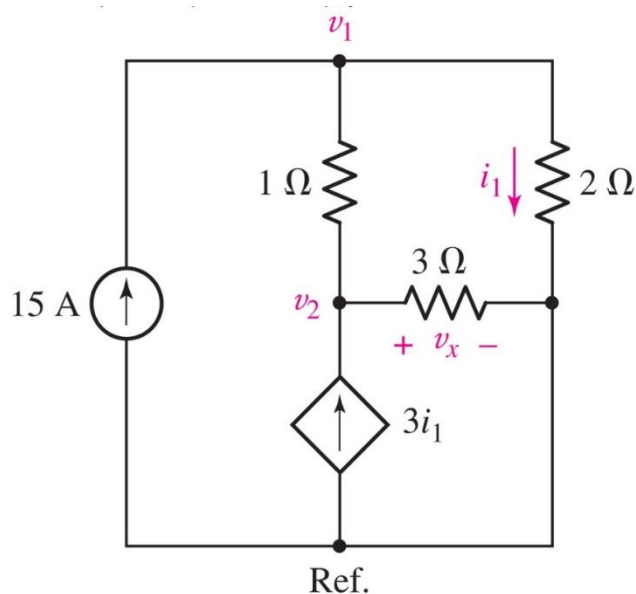Determine the power supplied by the dependent source.



Nodal Analysis: Dependent Source Example

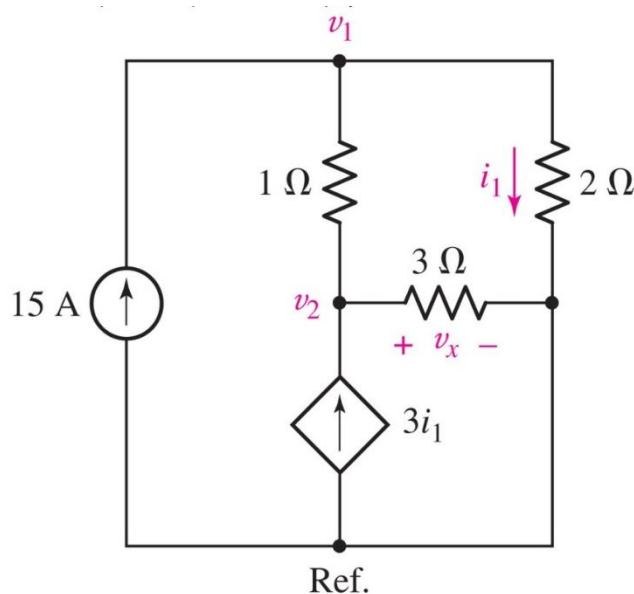
Determine the power supplied by the dependent source.



Key step: eliminate i_1 from the equations using $v_1 = 2i_1$

Nodal Analysis: Dependent Source Example

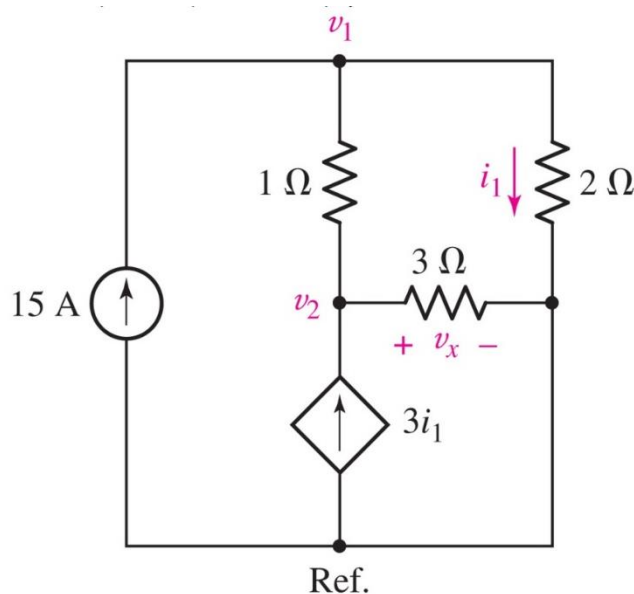Determine the power supplied by the dependent source.




Key step: eliminate i_1 from the equations using $v_1 = 2i_1$

Answer: 4.5 kW


Voltage Sources and the Super node

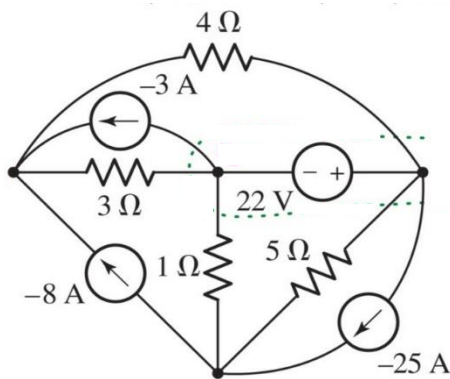What is the current through a voltage source connected between nodes?




Voltage Sources and the Super node

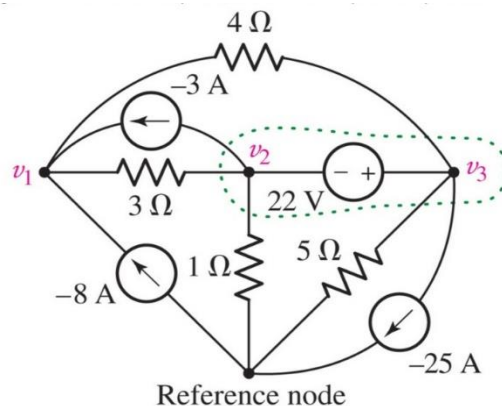What is the current through a voltage source connected between nodes?



Voltage Sources and the Super node

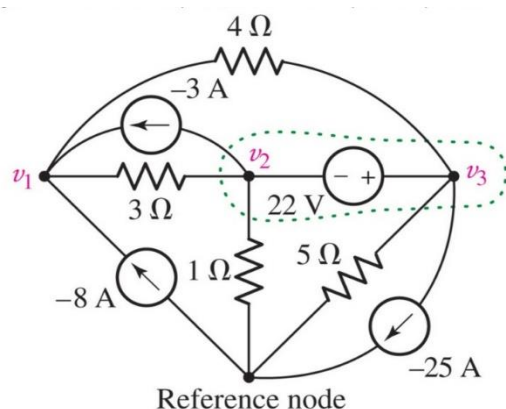
What is the current through a voltage source connected between nodes?




We can eliminate the need for introducing a current variable by applying **KCL** to the **super node**.

Voltage Sources and the Super node

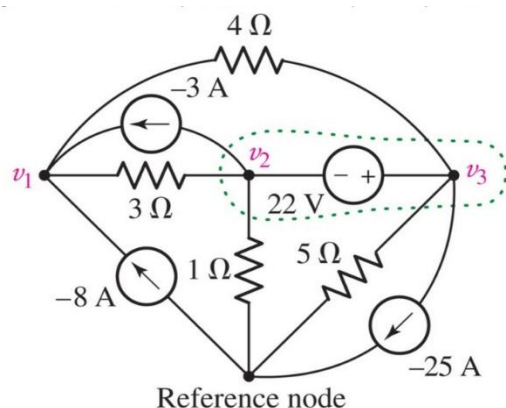
What is the current through a voltage source connected between nodes?



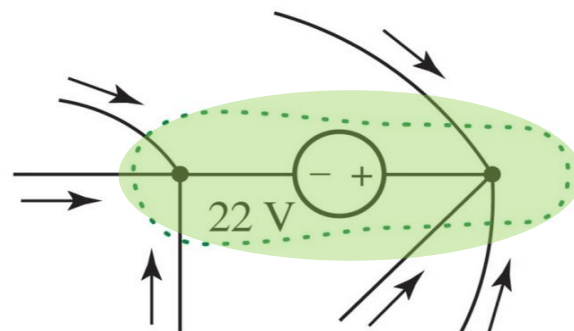
We can eliminate the need for introducing a current variable by applying KCL to the **super node**.



Super node

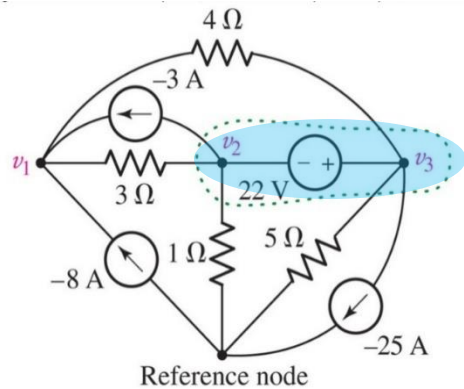

Super node

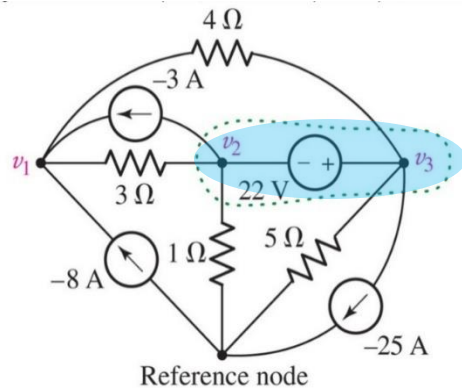


□ Apply KCL at Node 1.

$$-(-8) - (-3) + \frac{v_1 - v_3}{4} + \frac{v_1 - v_2}{3} = 0$$

$$-3 + \frac{v_2}{1} + \frac{v_2 - v_1}{3} + \frac{v_3}{5} + \frac{v_3 - v_1}{4} - 25 = 0$$

$$v_3 - v_2 = 22$$

Super node

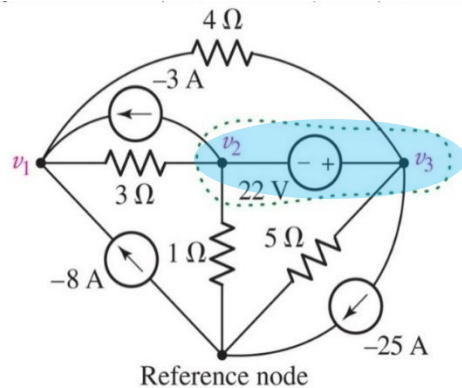

□ Apply KCL at Node 1.


□ Apply KCL at the super node.

$$-(-8) - (-3) + \frac{v_1 - v_3}{4} + \frac{v_1 - v_2}{3} = 0$$

$$-3 + \frac{v_2}{1} + \frac{v_2 - v_1}{3} + \frac{v_3}{5} + \frac{v_3 - v_1}{4} - 25 = 0$$

$$v_3 - v_2 = 22$$

Super node

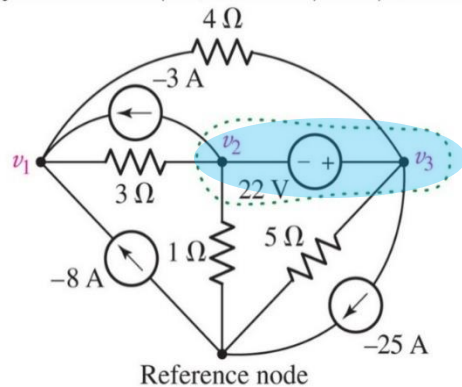

- Apply KCL at Node 1.
- Apply KCL at the super node.
- Add the equation for the voltage source inside the super node.


$$-(-8) - (-3) + \frac{v_1 - v_3}{4} + \frac{v_1 - v_2}{3} = 0$$

$$-3 + \frac{v_2}{1} + \frac{v_2 - v_1}{3} + \frac{v_3}{5} + \frac{v_3 - v_1}{4} - 25 = 0$$

$$v_3 - v_2 = 22$$


Example (With Dependent Source)

Find i_1 using Nodal Analysis

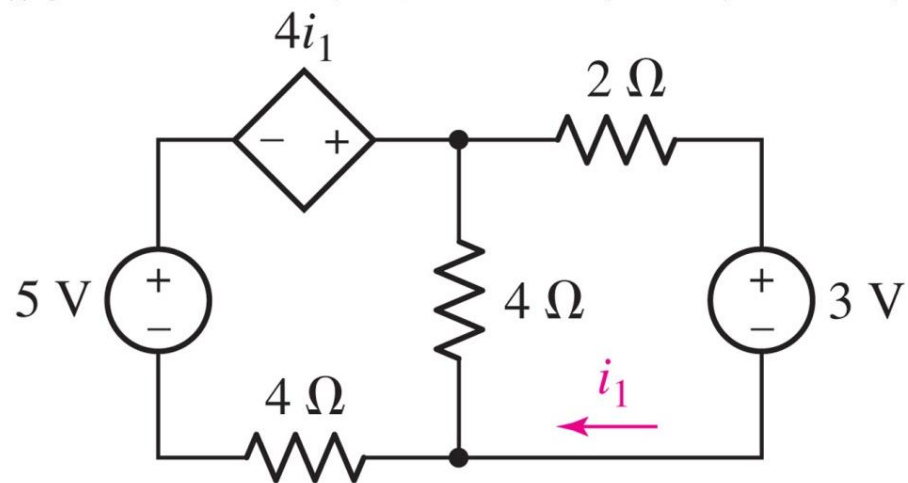

Example (With Dependent Source)

Find i_1 using Nodal Analysis

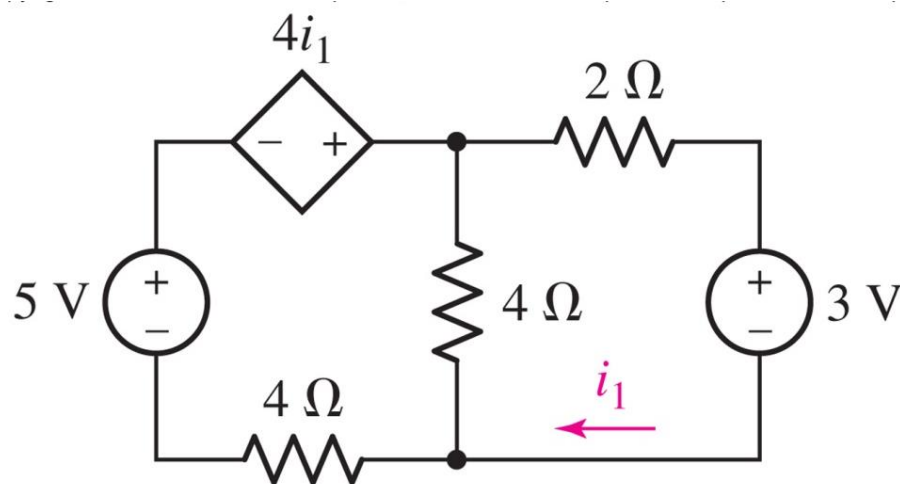


Answer: $i_1 = -250 \text{ mA}$

Mesh Analysis (Alternative)

- ❑ A mesh is a loop which does not contain any other loops within it.
- ❑ In mesh analysis, we assign currents to each mesh and solve them using KVL.
- ❑ Assigning mesh currents automatically ensures KCL is followed.


Mesh Analysis (Alternative)

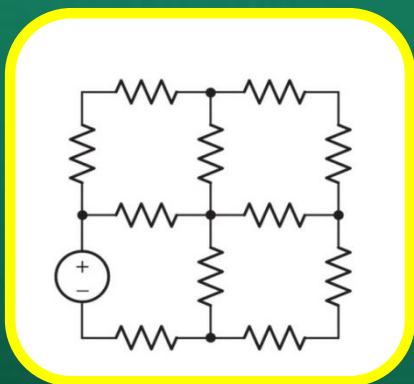- ❑ A mesh is a loop which does not contain any other loops within it.
- ❑ In mesh analysis, we assign currents to each mesh and solve them using KVL.
- ❑ Assigning mesh currents automatically ensures KCL is followed.




Mesh Analysis (Alternative)

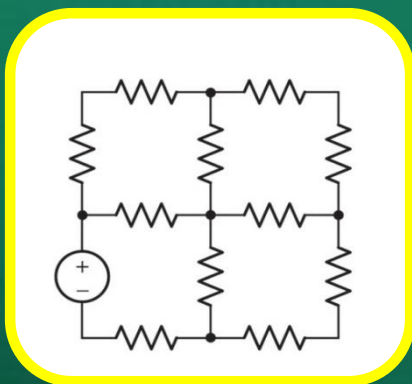- ❑ A mesh is a loop which does not contain any other loops within it.
- ❑ In mesh analysis, we assign currents to each mesh and solve them using KVL.
- ❑ Assigning mesh currents automatically ensures KCL is followed.




This circuit has 4 meshes.


The Mesh Analysis Method

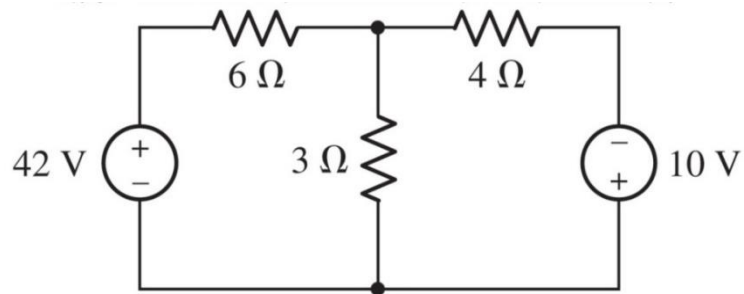


The Mesh Analysis Method

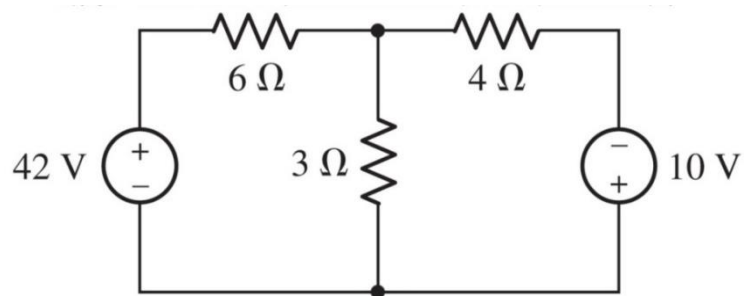



Mesh currents

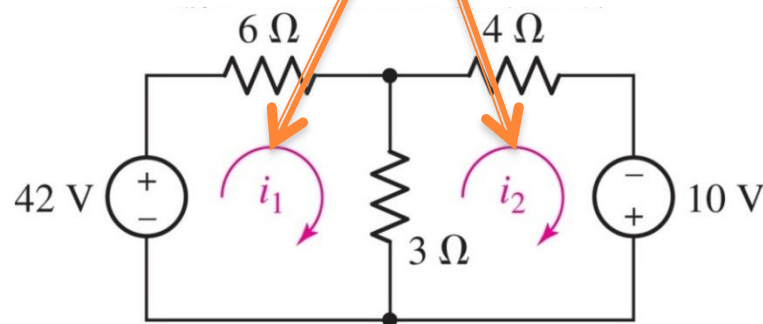

The Mesh Analysis Method

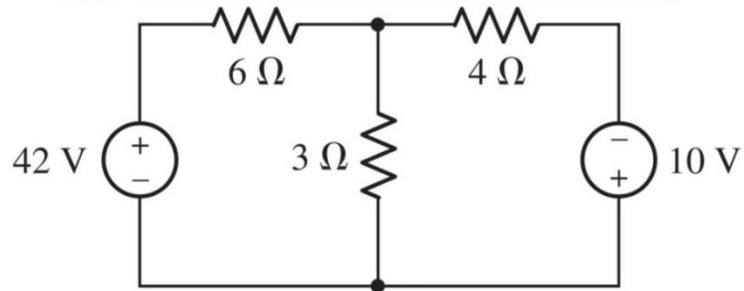


Mesh currents

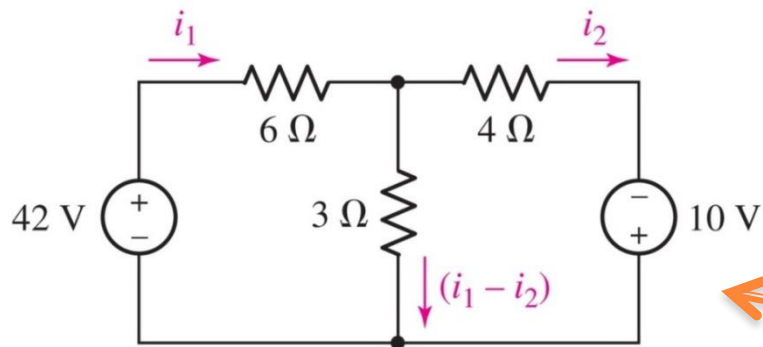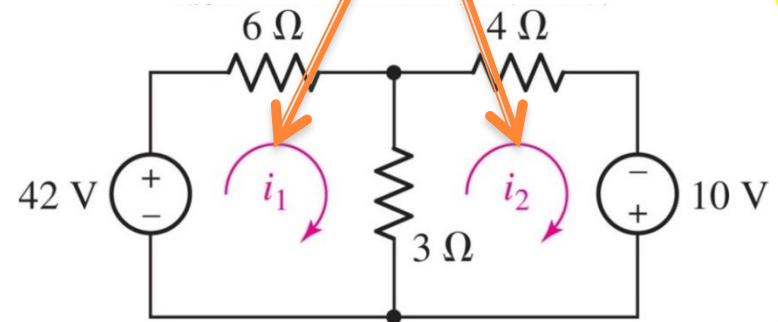


Branch currents

Mesh: Apply KVL

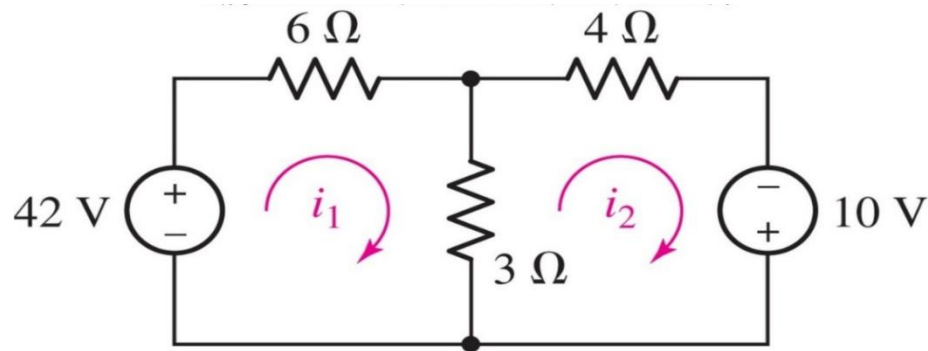


Mesh: Apply KVL

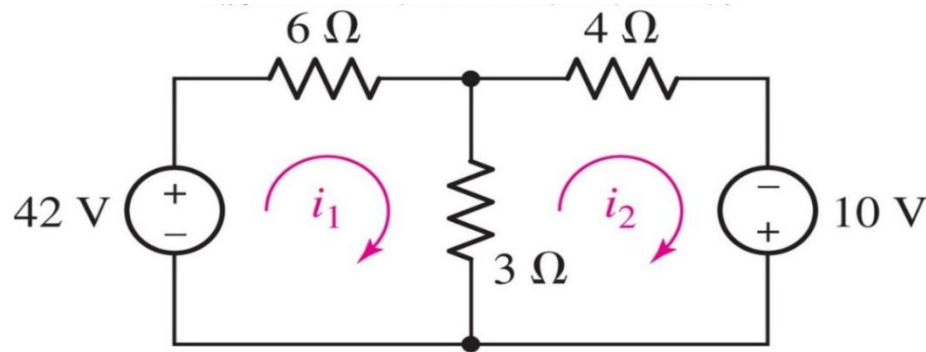

Apply KVL to mesh 1 (Σ drops = 0)

$$-42 + 6i_1 + 3(i_1 - i_2) = 0$$

Mesh: Apply KVL

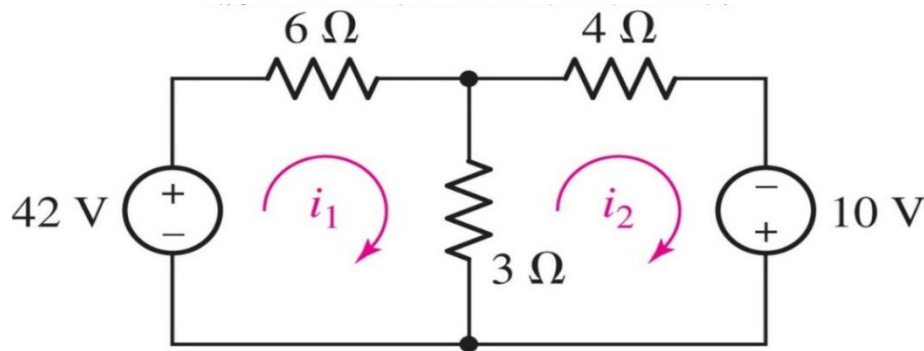

Apply KVL to mesh 1 (Σ drops = 0)


$$-42 + 6i_1 + 3(i_1 - i_2) = 0$$

Apply KVL to mesh 2 (Σ drops = 0)

$$3(i_2 - i_1) + 4i_2 - 10 = 0$$

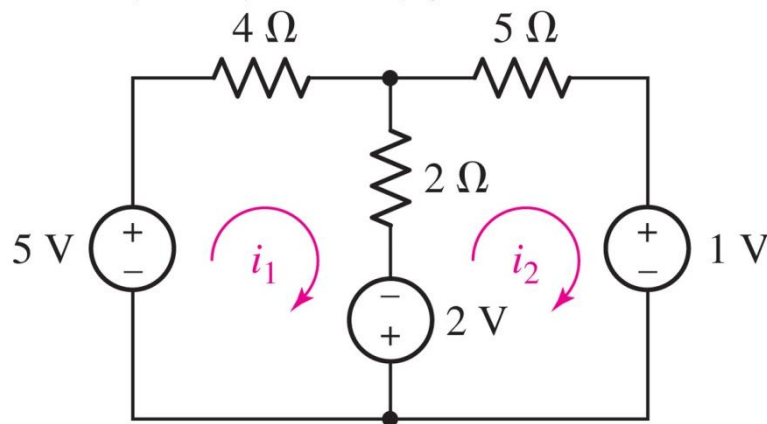
Example: Mesh Analysis

Determine the power supplied by the 2 V source.



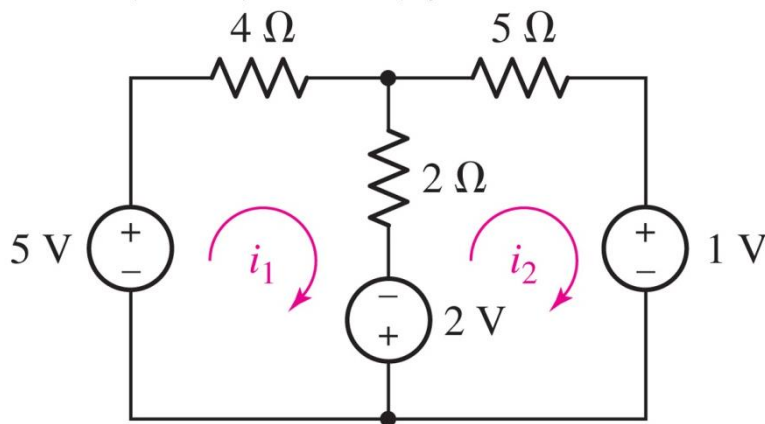Example: Mesh Analysis

Determine the power supplied by the 2 V source.




Applying KVL to the meshes

$$-5 + 4i_1 + 2(i_1 - i_2) - 2 = 0$$

$$+2 + 2(i_2 - i_1) + 5i_2 + 1 = 0$$

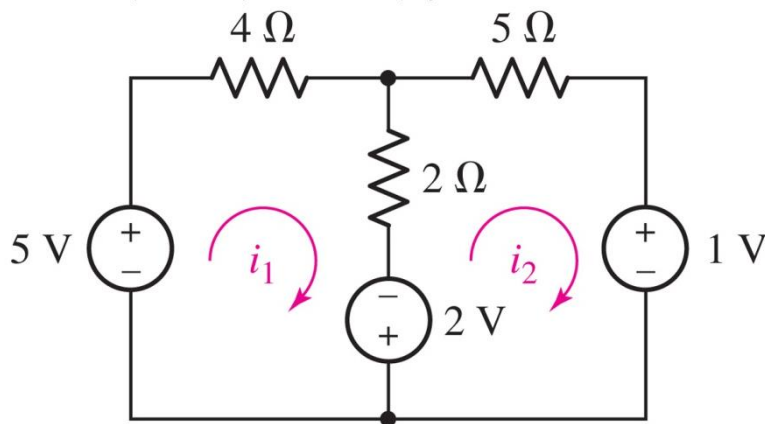Example: Mesh Analysis

Determine the power supplied by the 2 V source.



Applying KVL to the meshes


$$-5 + 4i_1 + 2(i_1 - i_2) - 2 = 0$$

$$+2 + 2(i_2 - i_1) + 5i_2 + 1 = 0$$

$$i_1 = 1.1316 \text{ A}, i_2 = -0.1053 \text{ A}$$

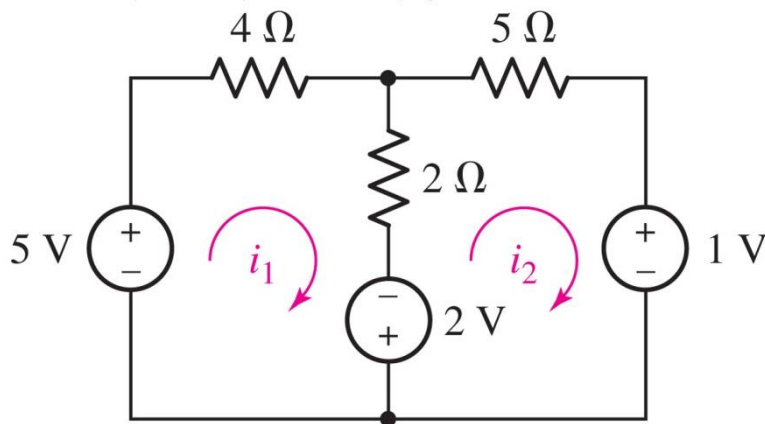Example: Mesh Analysis

Determine the power supplied by the 2 V source.



Applying KVL to the meshes

$$-5 + 4i_1 + 2(i_1 - i_2) - 2 = 0$$


$$+2 + 2(i_2 - i_1) + 5i_2 + 1 = 0$$

$$i_1 = 1.1316 \text{ A}, i_2 = -0.1053 \text{ A}$$

$$P_{2V} = (i_2 - i_1) \times 2 = -2.4746 \text{ W}$$

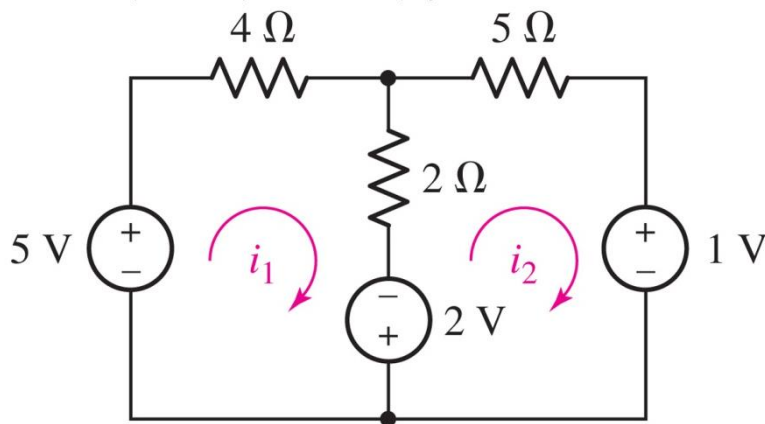Example: Mesh Analysis

Determine the power supplied by the 2 V source.



Applying KVL to the meshes


$$-5 + 4i_1 + 2(i_1 - i_2) - 2 = 0$$

$$+2 + 2(i_2 - i_1) + 5i_2 + 1 = 0$$


$$i_1 = 1.1316 \text{ A}, i_2 = -0.1053 \text{ A} \quad P_{2V} = (i_2 - i_1) \times 2 = -2.4746 \text{ W}$$

Answer: Power supplied by 2V source is 2.4738 W

A Three Mesh Example

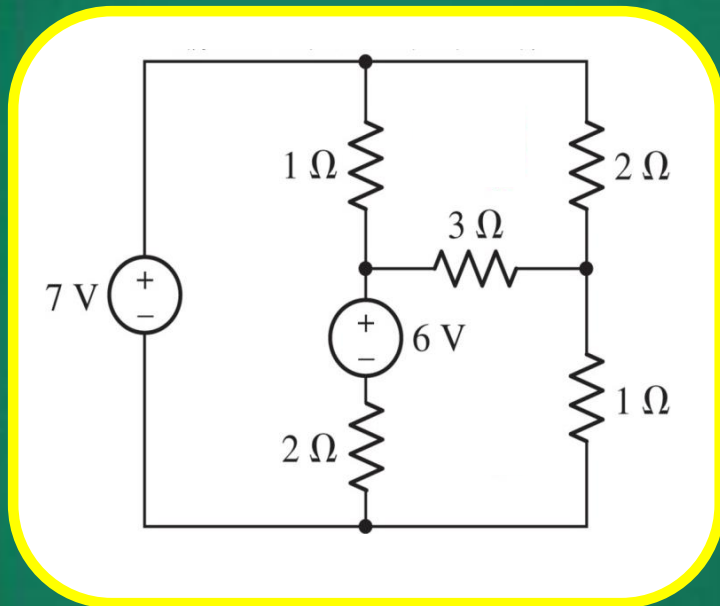


A Three Mesh Example

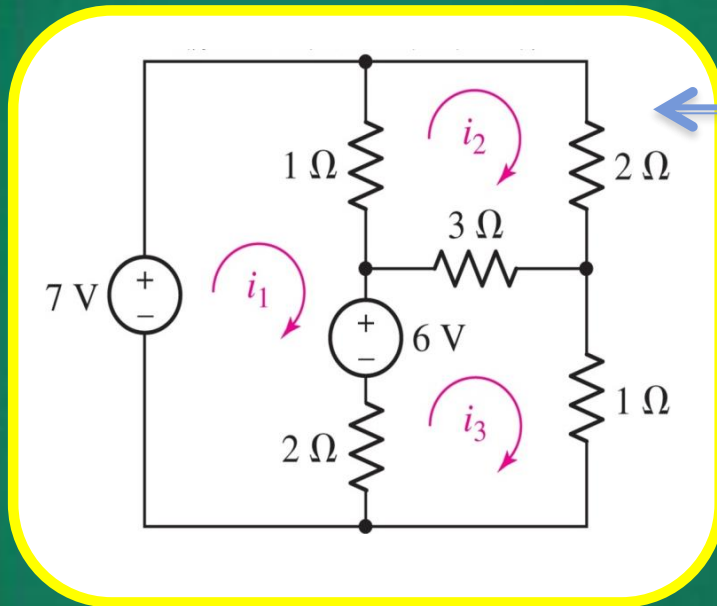

Follow each mesh clockwise

A Three Mesh Example

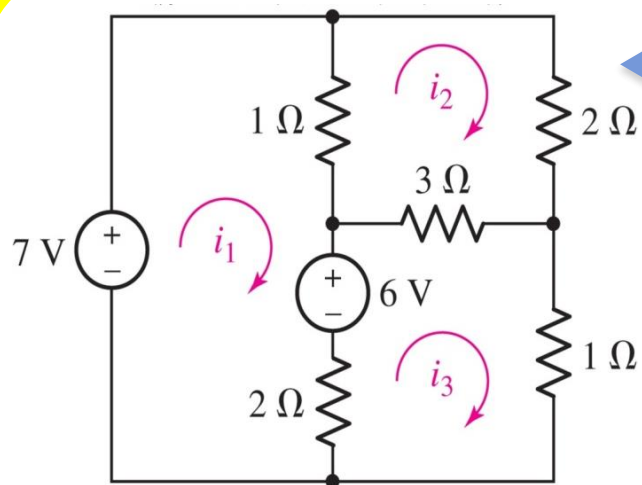


Follow each mesh clockwise

$$-7 + 1(i_1 - i_2) + 6 + 2(i_1 - i_3) = 0$$

$$1(i_2 - i_1) + 2i_2 + 3(i_2 - i_3) = 0$$

$$2(i_3 - i_1) - 6 + 3(i_3 - i_2) + 1i_3 = 0$$

A Three Mesh Example

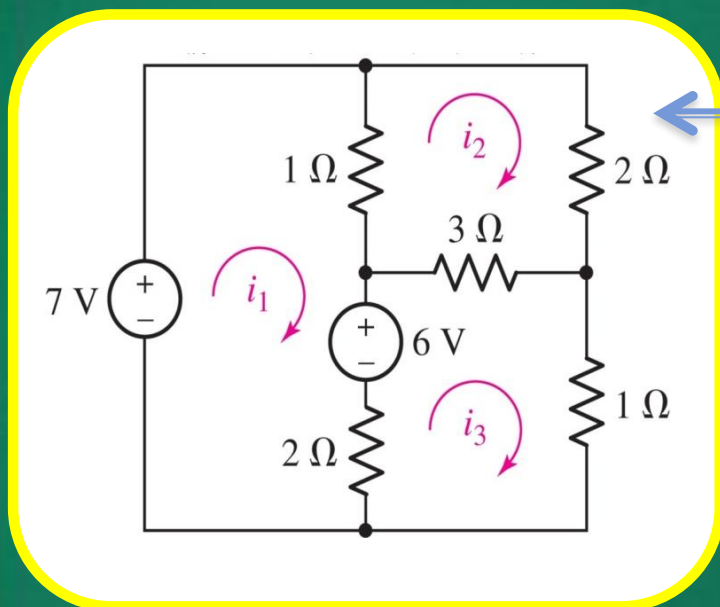

Follow each mesh clockwise

$$-7 + 1(i_1 - i_2) + 6 + 2(i_1 - i_3) = 0$$

$$1(i_2 - i_1) + 2i_2 + 3(i_2 - i_3) = 0$$

$$2(i_3 - i_1) - 6 + 3(i_3 - i_2) + 1i_3 = 0$$

On simplification

$$+3i_1 - i_2 - 2i_3 = 1$$

$$-i_1 + 6i_2 - 3i_3 = 0$$

$$-2i_1 - 3i_2 + 6i_3 = 6$$

A Three Mesh Example

Equations in matrix form

A Three Mesh Example

Equations in matrix form

$$\begin{bmatrix} 3 & -1 & -2 \\ -1 & 6 & -3 \\ -2 & -3 & 6 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 1 \\ 0 \\ 6 \end{bmatrix}$$

A Three Mesh Example

Equations in matrix form

$$\begin{bmatrix} 3 & -1 & -2 \\ -1 & 6 & -3 \\ -2 & -3 & 6 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 1 \\ 0 \\ 6 \end{bmatrix}$$

A

A Three Mesh Example

Equations in matrix form

$$\begin{bmatrix} 3 & -1 & -2 \\ -1 & 6 & -3 \\ -2 & -3 & 6 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 1 \\ 0 \\ 6 \end{bmatrix}$$

A I

A Three Mesh Example

Equations in matrix form

$$\begin{bmatrix} 3 & -1 & -2 \\ -1 & 6 & -3 \\ -2 & -3 & 6 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 1 \\ 0 \\ 6 \end{bmatrix}$$

$A \qquad I \qquad B$

A Three Mesh Example

Equations in matrix form

$$\begin{bmatrix} 3 & -1 & -2 \\ -1 & 6 & -3 \\ -2 & -3 & 6 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 1 \\ 0 \\ 6 \end{bmatrix}$$

$A \qquad I \qquad B$

$$I = A^{-1} \times B$$

A Three Mesh Example

Equations in matrix form

$$\begin{bmatrix} 3 & -1 & -2 \\ -1 & 6 & -3 \\ -2 & -3 & 6 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 1 \\ 0 \\ 6 \end{bmatrix}$$


$A \qquad I \qquad B$

$$I = A^{-1} \times B$$

Answer: $i_1 = 3, i_2 = 3, i_3 = 3$


Current Sources and Supermesh

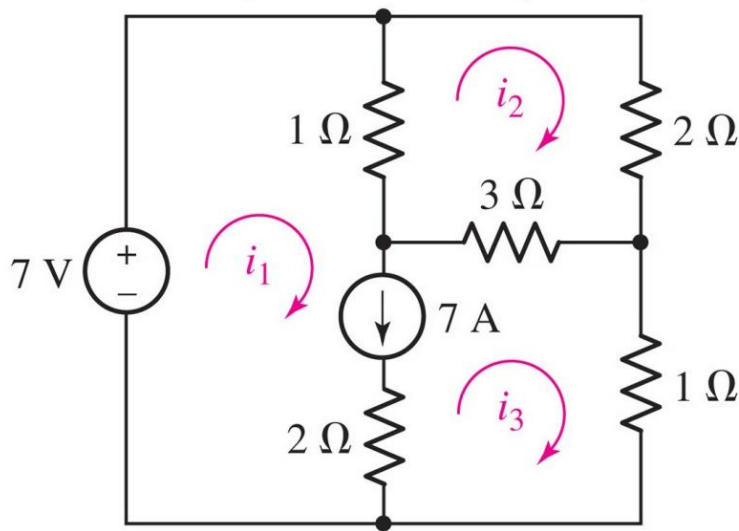What is the voltage across a current source in between two meshes?



Current Sources and Supermesh

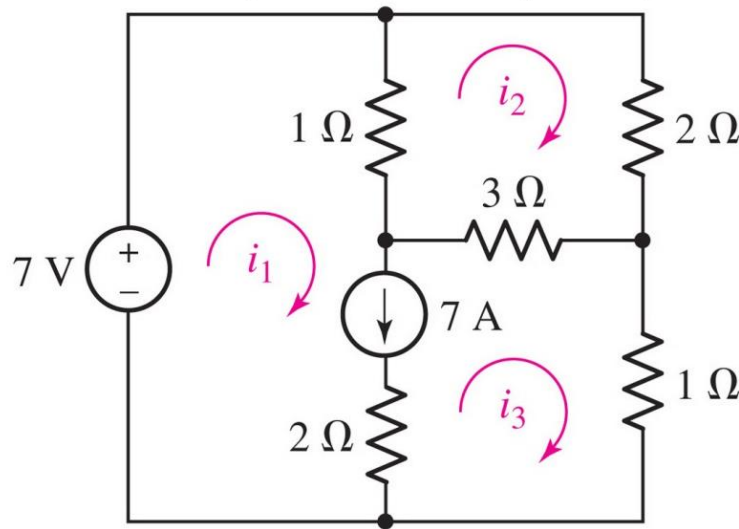
What is the voltage across a current source in between two meshes?



We can eliminate the need for introducing a voltage variable by applying **KVL** to the **super mesh** formed by joining **mesh 1** and **mesh 3**.


Current Sources and Supermesh

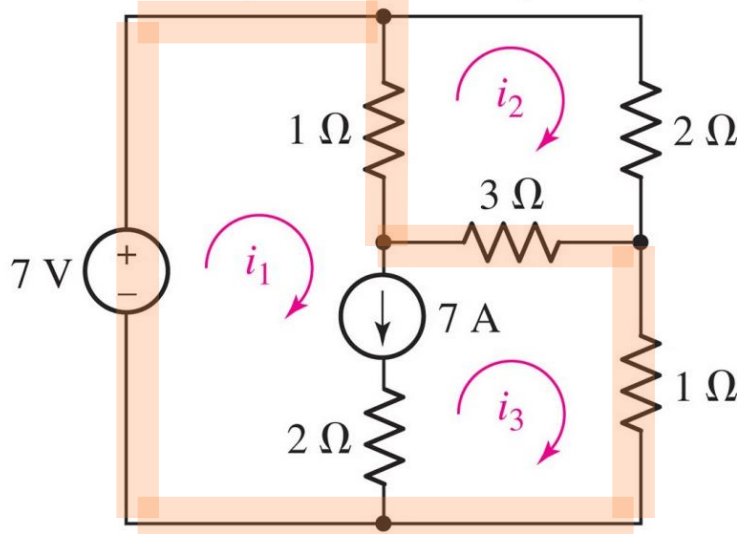What is the voltage across a current source in between two meshes?




We can eliminate the need for introducing a voltage variable by applying **KVL** to the **super mesh** formed by joining **mesh 1** and **mesh 3**.

Super mesh

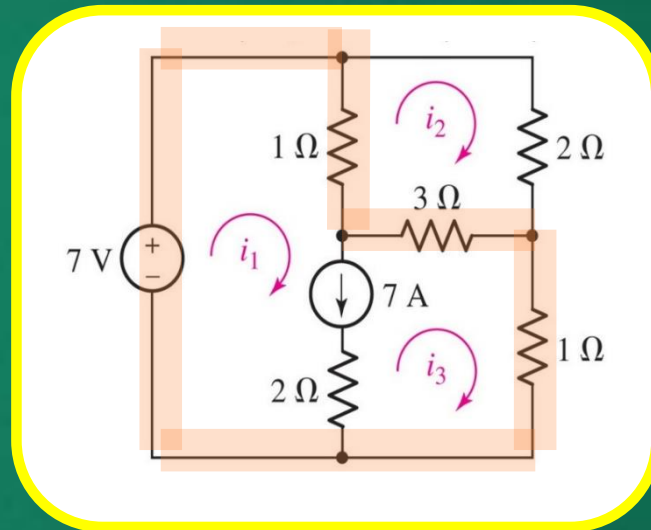


Super mesh

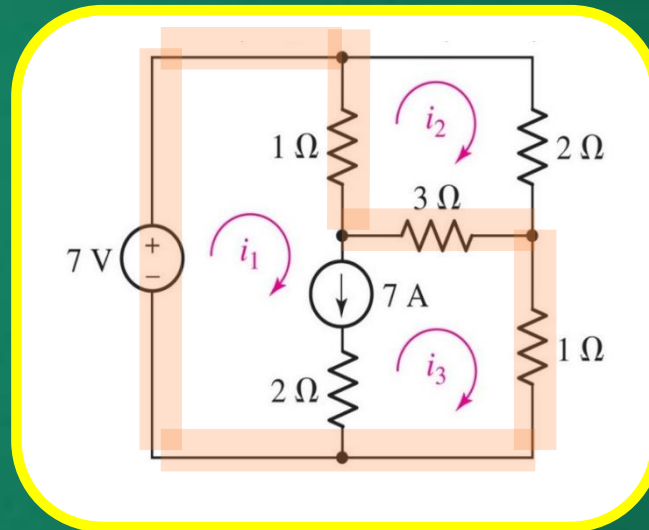

Apply KVL to mesh 2:

$$1(i_2 - i_1) + 2i_2 + 3(i_2 - i_3)$$

Super mesh

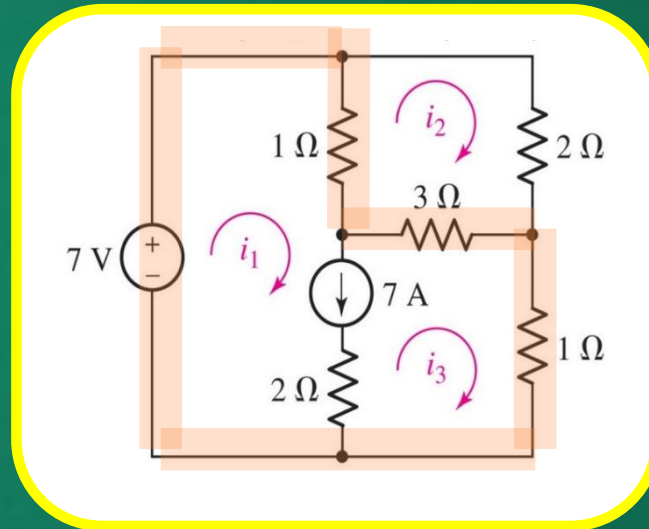


Apply KVL to mesh 2: $1(i_2 - i_1) + 2i_2 + 3(i_2 - i_3)$

Apply KVL supermesh 1/3:

$$-7 + 1(i_1 - i_2) + 3(i_3 - i_2) + 1i_3$$

Super mesh

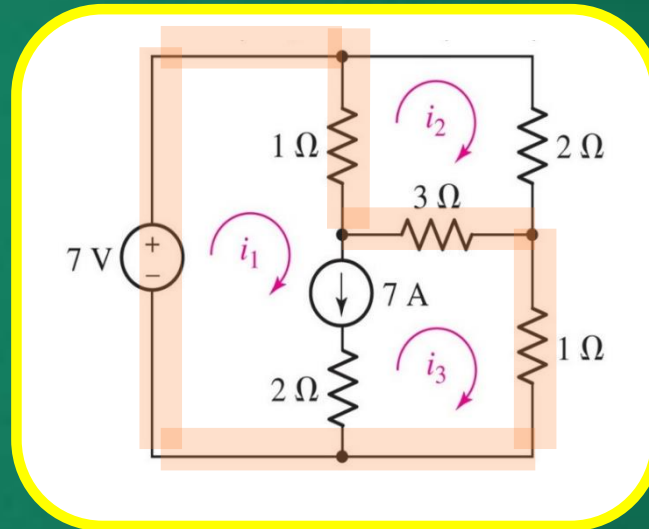


Apply KVL to mesh 2: $1(i_2 - i_1) + 2i_2 + 3(i_2 - i_3)$

Apply KVL supermesh 1/3:

$$-7 + 1(i_1 - i_2) + 3(i_3 - i_2) + 1i_3$$

Add the current source: $i_1 - i_3 = 7$

Super mesh

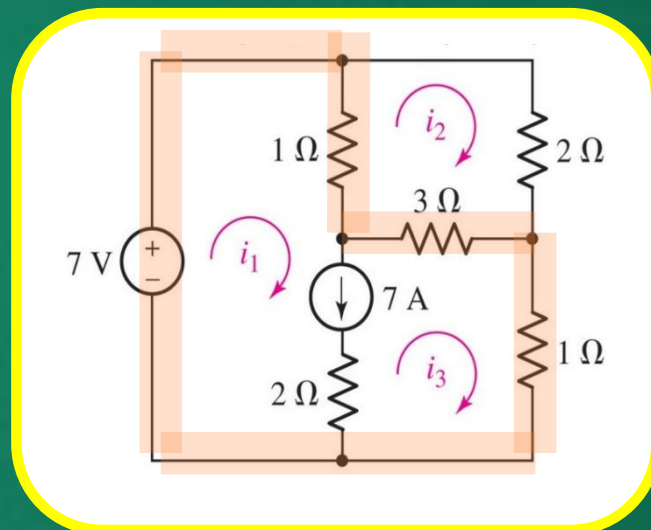


$$-i_1 + 6i_2 - 3i_3 = 0$$

$$i_1 - 4i_2 + 4i_3 = 7$$

$$i_1 - i_3 = 7$$

Super mesh

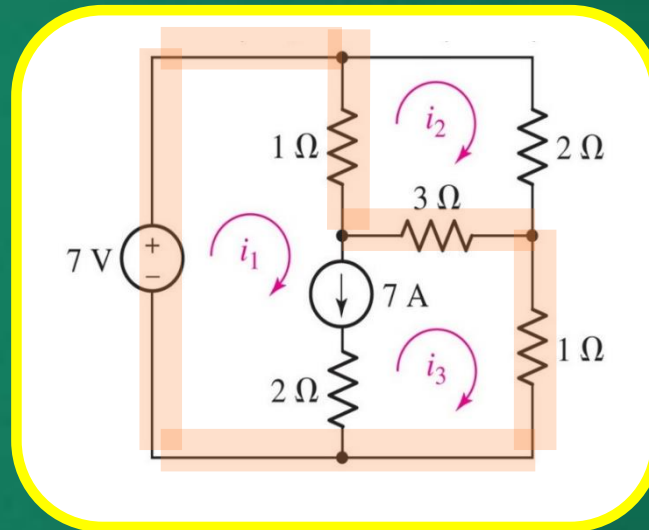

$$-i_1 + 6i_2 - 3i_3 = 0$$


$$i_1 - 4i_2 + 4i_3 = 7$$

$$i_1 - i_3 = 7$$

Answer: $i_1 = 9$, $i_2 = 2.5$, $i_3 = 2$

Dependent Source Example

Compute all the mesh currents.

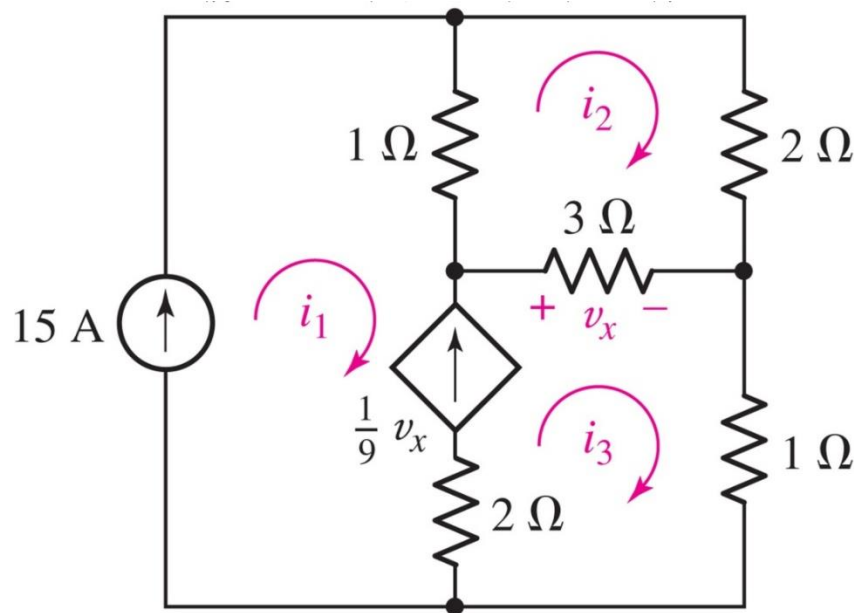

Dependent Source Example

In mesh 1:

$$i_1 = 15$$

Dependent Source Example

In mesh 1:

$$i_1 = 15$$

In mesh 2:

$$i_3 - i_1 = \frac{V_x}{9} \implies i_3 - 15 = \frac{V_x}{9}$$

Dependent Source Example

In mesh 1:

$$i_1 = 15$$

In mesh 2:

$$i_3 - i_1 = \frac{V_x}{9} \implies i_3 - 15 = \frac{V_x}{9}$$

Apply KVL to mesh 2

$$1(i_2 - i_1) + 2i_2 + 3(i_2 - i_3) = 0$$

Dependent Source Example

In mesh 1:

$$i_1 = 15$$

In mesh 2:

$$i_3 - i_1 = \frac{V_x}{9} \implies i_3 - 15 = \frac{V_x}{9}$$

Apply KVL to mesh 2

$$1(i_2 - i_1) + 2i_2 + 3(i_2 - i_3) = 0$$

$$\implies i_2 - 15 + 2i_2 + 3(i_2 - i_3) = 0$$

Dependent Source Example

In mesh 1:

$$i_1 = 15$$

In mesh 2:

$$i_3 - i_1 = \frac{V_x}{9} \implies i_3 - 15 = \frac{V_x}{9}$$

Apply KVL to mesh 2

$$1(i_2 - i_1) + 2i_2 + 3(i_2 - i_3) = 0$$

$$\implies i_2 - 15 + 2i_2 + 3(i_2 - i_3) = 0$$

$$v_x = 3(i_3 - i_2)$$

Dependent Source Example

$$\begin{aligned}i_1 &= 15 \\6i_2 - 3i_3 &= 15 \\3i_2 + 6i_3 &= 135\end{aligned}$$

Answer: $i_1 = 15, i_2 = 11, i_3 = 17$

Node or Mesh: How to Choose?

- ☐ **Use the one with fewer equations, or**
- ☐ **Use the method you like best, or**
- ☐ **Use both (as a check)**

Example

Use both Nodal and Mesh Analysis to find v_1

