

Problem Sheet - 1

IEC102

Q1) A 2-terminal device consumes energy as shown by the waveform in Fig. Q1. The current through the device is $i(t) = 2 \cos(4000\pi t)$ A. Find the voltage across the device at $t = 0.5, 1.5, 4.75$, and 6.5 ms.

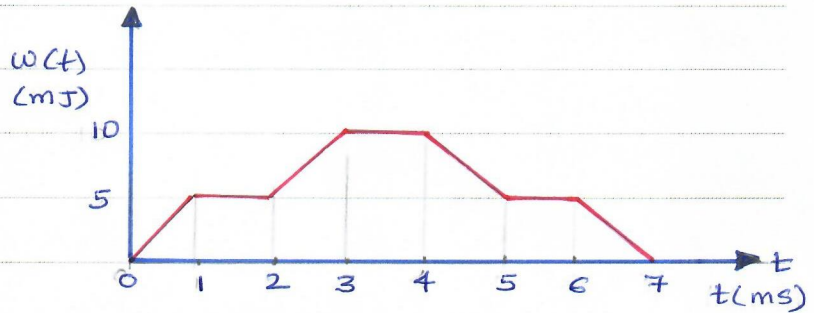
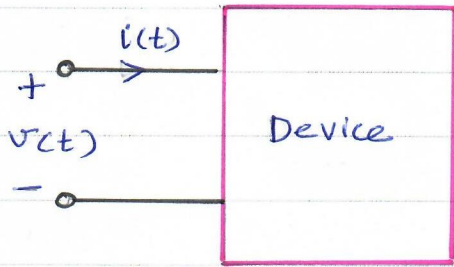


Fig. Q1

Q2 Find the power absorbed or supplied by the element 3 of the circuit shown in Fig. Q2

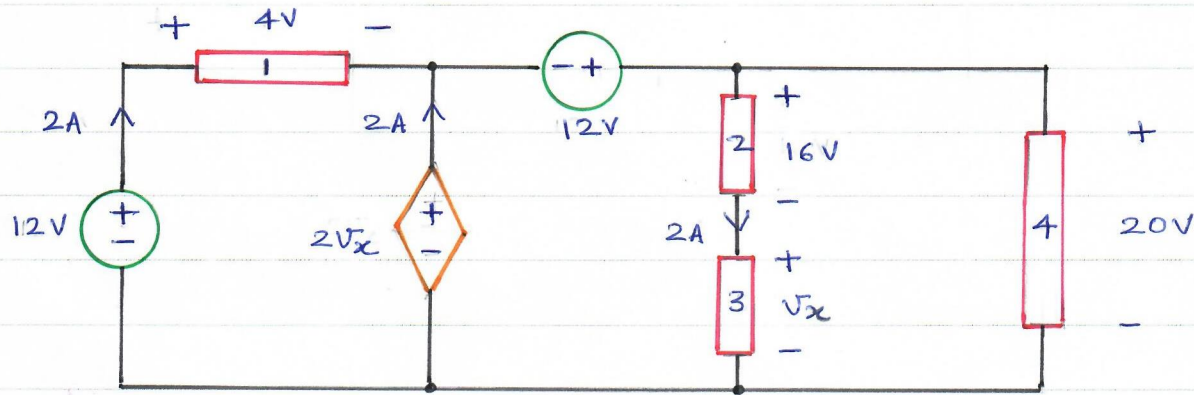


Fig. Q2

Q3 In the circuit shown in Fig. Q3, compute the power delivered or absorbed by the dependent source.

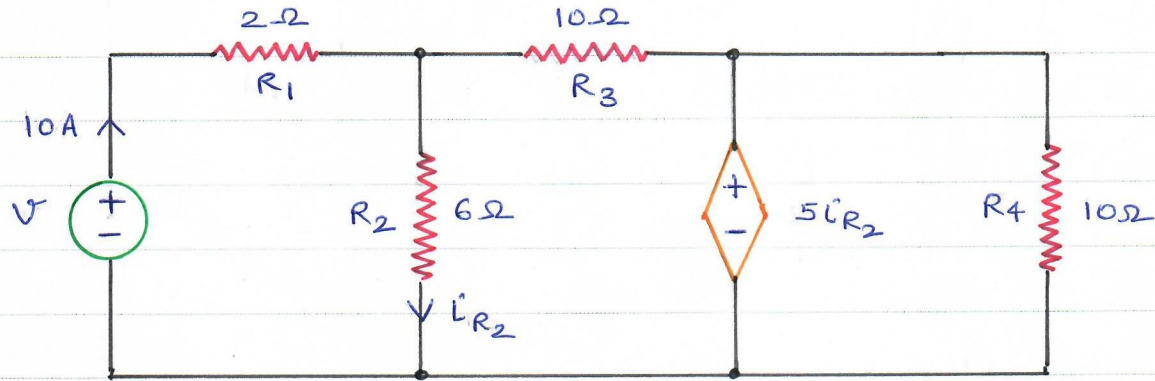


Fig. Q3

Q4 Find V_0 in the circuit shown in Fig. Q4.

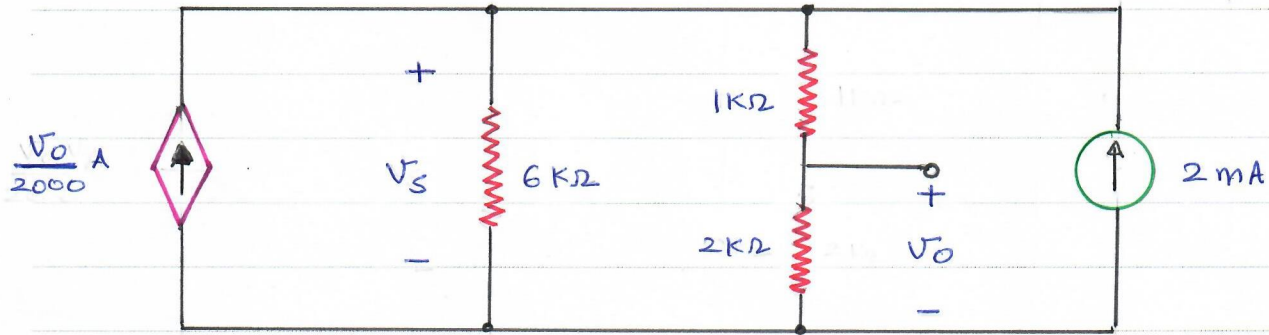


Fig. Q4