

Solutions to Problem Sheet-3

IEC102

Q1) Apply the superposition principle to find V_0 in the circuit shown in Fig. Q1

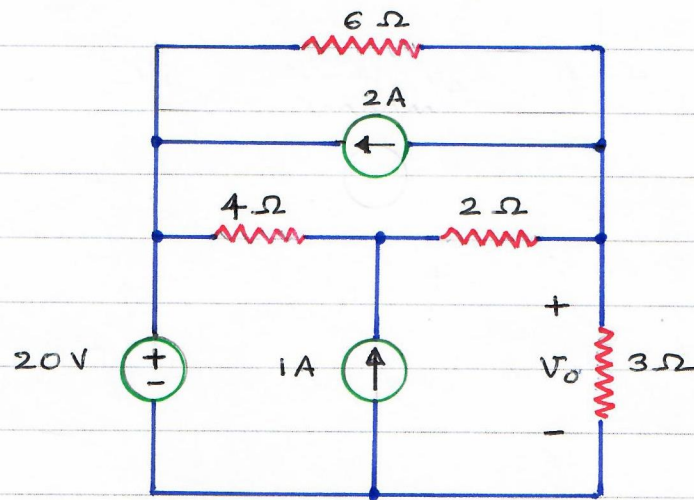


Fig. Q1

Sol.



Let V_{01} be the voltage across 3Ω resistor due to $20V$ source acting alone.

Similarly, let V_{02} and V_{03} be the voltage across 3Ω resistor due to $2A$ and $1A$ current sources acting independently.

By superposition $V_0 = V_{01} + V_{02} + V_{03}$

V_{01}

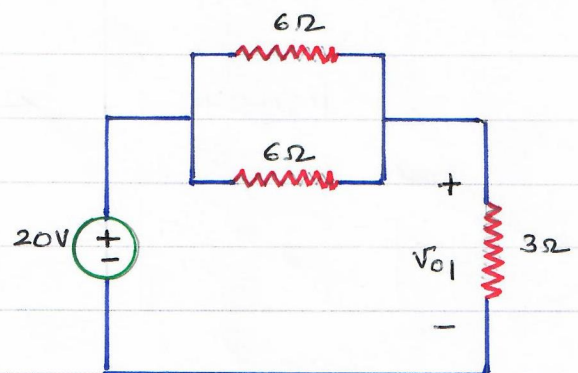
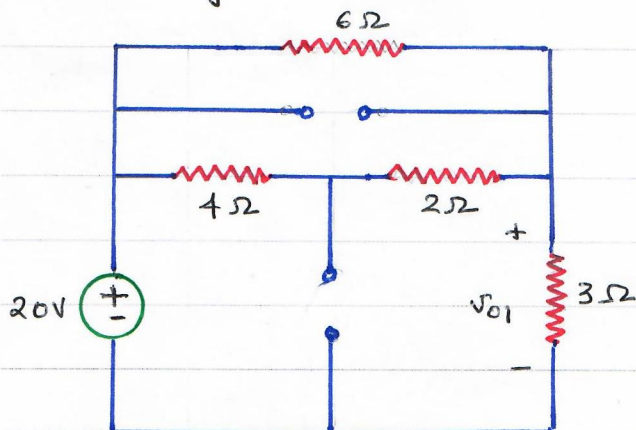
When only $20V$ source is there and other sources are disabled.



$$V_{01} = \frac{20 \times 3}{6 + 3} = \frac{20 \times 3}{9} = 10V$$

V_{02}

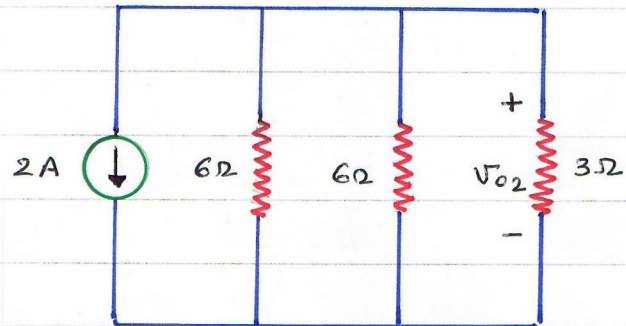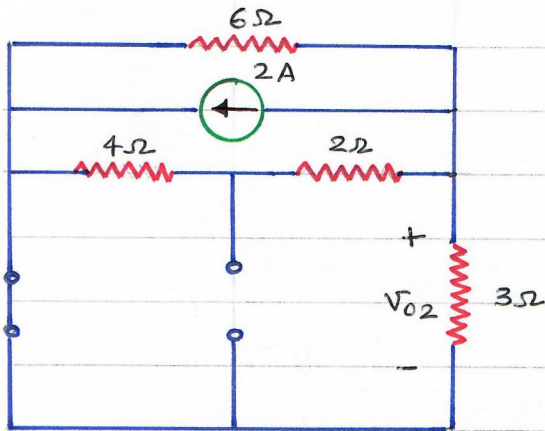When only 2A current source is acting and other sources are disabled.





$$V_{02} = - 2 \times \frac{6 \parallel 6}{6 \parallel 6 + 3} \times 3$$

$$= - 2 \times \frac{3}{3+3} \times 3$$

$$\Rightarrow V_{02} = -3V$$

V_{03}

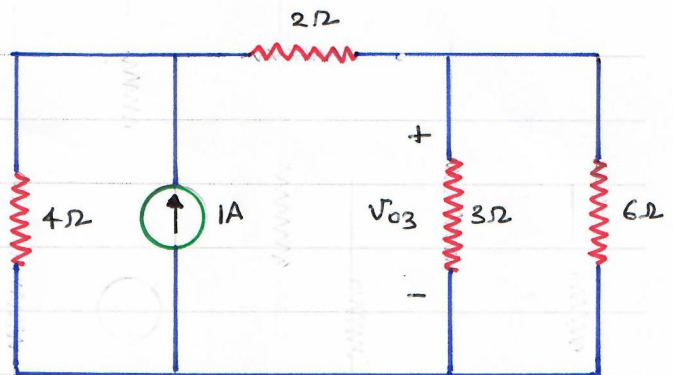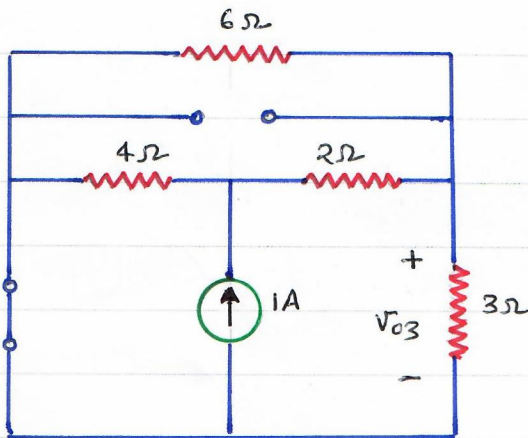

$$V_{03} = 1 \times \frac{4}{4 + 2 + 3 \parallel 6} \times (3 \parallel 6)$$

$$= \frac{4}{4+2+2} \times 2 = \frac{4}{8} \times 2 = 1V$$

When all the sources are acting the voltage across 3Ω resistor = $V_0 = V_{01} + V_{02} + V_{03} = 10 - 3 + 1 = 8V$

(Q2) Find the Thevenin & Norton equivalent circuit at terminals a-b of the circuit shown in Fig. Q2


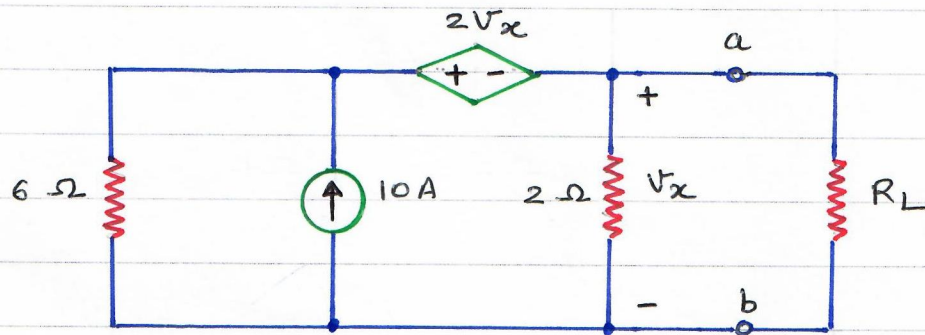


Fig. Q2

Sol.

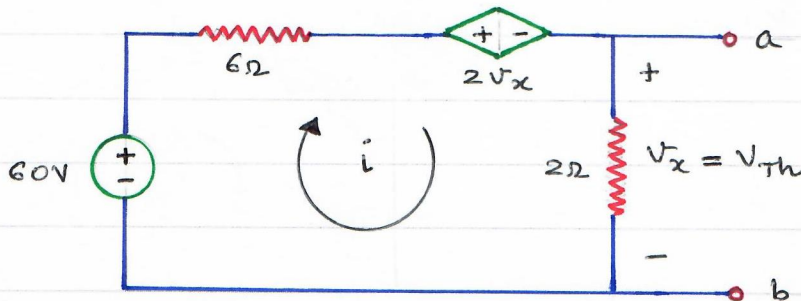Using source transformation on 10A current source in parallel with 6Ω resistor.



Applying KVL around loop


$$-60 + 6i + 2V_x + V_x = 0$$

$$V_x = 2i$$

$$\Rightarrow i = V_x / 2$$

$$-60 + 6 \frac{V_x}{2} + 2V_x + V_x = 0$$
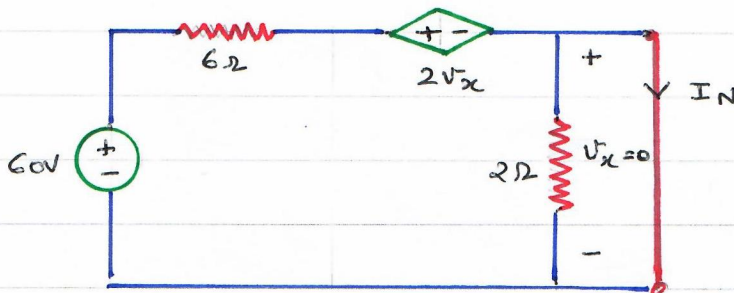
$$\Rightarrow 6V_x = 60 \Rightarrow V_x = V_{Th} = 10V$$





$$-60 + 6I_N + 2V_x = 0$$

$$\Rightarrow -60 + 6I_N = 0 \quad (\because V_x = 0)$$

$$\Rightarrow I_N = 10A$$

$$R_{eq} = R_{Th} = R_N = \frac{V_{Th}}{I_N} = \frac{10}{10} = 1\Omega$$

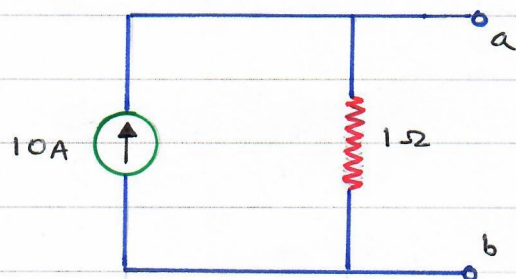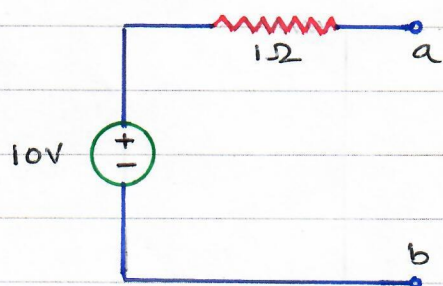Theremin and Norton equivalent circuits are



Q3 Determine the Thevenin equivalent of the circuit shown in Fig. Q3

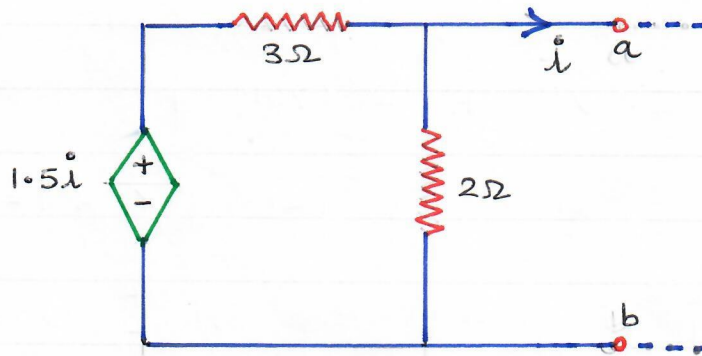


Fig. Q3


Sol.

$$V_{Th} = I_N = 0 \quad (\text{Since there are no independent sources})$$

R_{Th}

Insert a known test source at the terminals and find out the ratio of voltage to current to find R_{Th} .

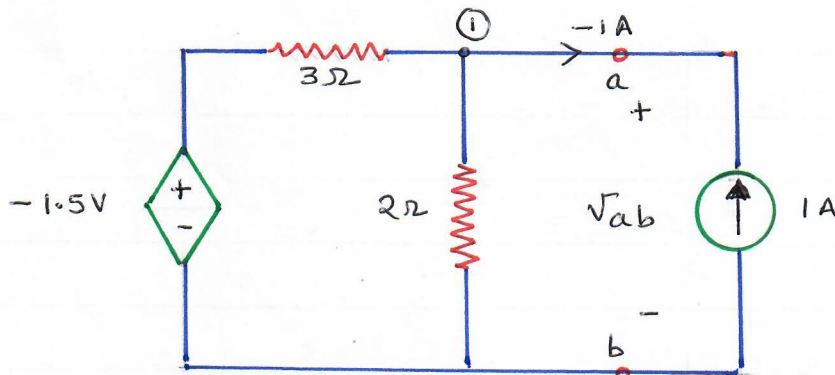Let us connect a test ^{current} source of 1A



$$R_{Th} = \frac{V_{ab}}{1}$$

$$V_{ab} =$$

Applying KCL at node (1)


$$\frac{V_{ab} - (-1.5)}{3} + \frac{V_{ab}}{2} - 1 = 0$$

$$\Rightarrow V_{ab} \left(\frac{1}{3} + \frac{1}{2} \right) = 1 - \frac{-1.5}{3} = 1 - 0.5 = 0.5$$

$$\Rightarrow V_{ab} \times \frac{5}{6} = 0.5 \quad ; \quad \Rightarrow V_{ab} = 0.6V$$

$$\therefore R_{Th} = 0.6\Omega$$

Thevenin equivalent circuit is

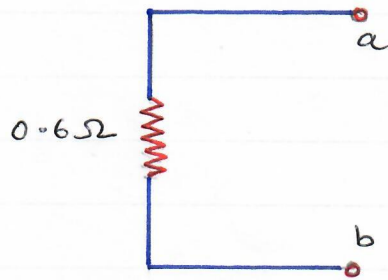

Q4 Find the value of R_L for maximum power transfer in the circuit shown in Fig. Q4. Also, find the maximum power dissipated in R_L .


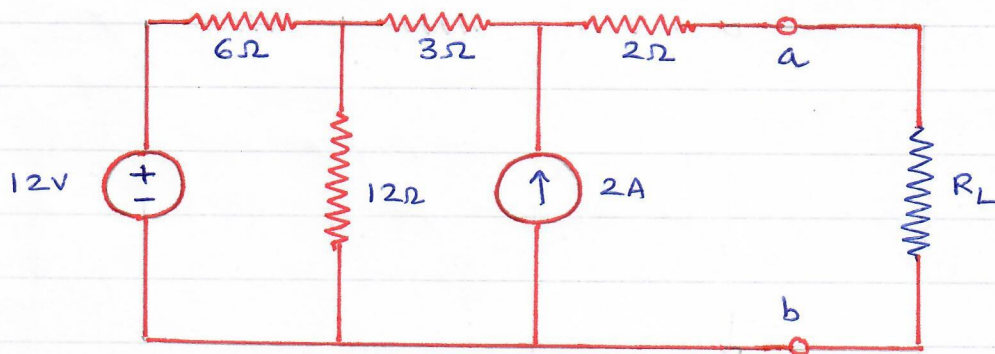


Fig. Q4

Sol.

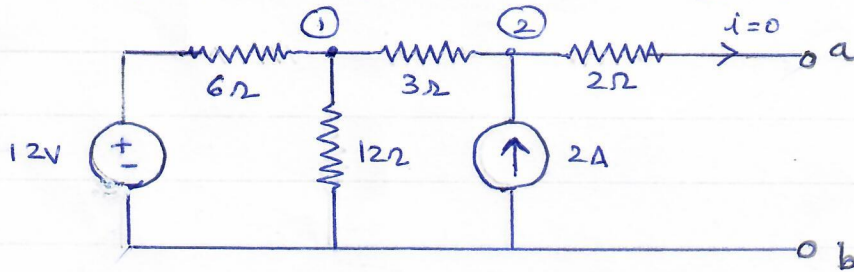Thereminize the circuit across terminals of R_L .



V_{th}

Applying KCL at node (1)

$$\frac{V_1 - 12}{6} + \frac{V_1}{12} + \frac{V_1 - V_2}{3} = 0$$

$$\Rightarrow \frac{2(V_1 - 12) + V_1 + 4(V_1 - V_2)}{12} = 0$$

$$\Rightarrow 7V_1 - 4V_2 = 24 \quad \dots (A)$$

Applying KCL at node (2)

$$-2 + \frac{V_2 - V_1}{3} = 0$$


$$\Rightarrow V_2 - V_1 = 6 \quad \dots (B)$$

Solving (A) and (B)

$$\boxed{V_2 = 22V = V_{th}}$$

$$\underline{R_{th}} = R_{eq}$$

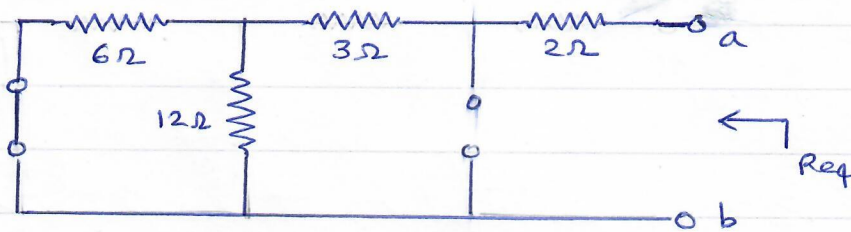
Turning off all the sources and calculating equivalent resistance across terminals a-b.



$$R_{eq} = R_{th} = 2 + 3 + 6 \parallel 12$$

$$= 2 + 3 + 4 = 9\Omega$$

Thevenin equivalent circuit

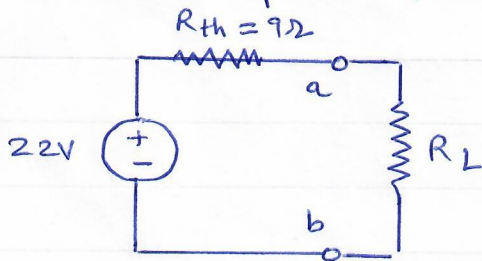

Maximum power is transferred to R_L when $R_L = R_{th} = 9\Omega$

Maximum power transferred to R_L when $R_L = R_{th} = 9\Omega$

$$P_{max \text{ in } R_L} = \left[\frac{22}{(9+9)} \right]^2 \times 9$$

$$= \left(\frac{11}{9} \right)^2 \times 9$$

$$\Rightarrow P_{max} = \left(\frac{11}{9} \right)^2 \times 9 = \frac{11 \times 11}{9} = \frac{121}{9} = 13.44 \text{ W}$$